

Application NoteServo Demultiplexer

AN-CM-280

Abstract

This application note describes how to create a model servo motor signal demultiplexer using a GreenPAK IC.

This application note comes complete with design files which can be found in the References section.



Contents

Ab	ostract	1
Сс	ontents	3
Fig	gures	3
Та	ables	3
1	Terms and Definitions	
2	References	
3	Introduction	
4	Servo Motor 1 RFChannel Multiplex	
-	•	
5	GreenPAK Design Schematic	
	5.1 GreenPAK Timing Blocks	
	5.2 GreenPAK ASM	9
6	GreenPAK Design Pinout	11
7	Test Results	12
8	Conclusion and Results Discussion	13
Αr	opendix A Source Code	14
•	evision History	
Ne	evision mistory	10
Fi	igures	
Fic	gure 1: SG90 Model Servo Motor	F
	gure 2: Time Multiplex – 8x 90° @ 50kS/s	
Fiç	gure 3: Time Multiplex – 7x 90°, #5 =0° @ 50kS/s	7
Fiç	gure 4: Top View of the GreenPAK Design Schematic	8
	gure 5: Close-up of Timing Blocks Settings	
	gure 6: Close View of ASM Settings	
	gure 7: Pin Configuration - STQFN20L	
	gure 8: Input/Output - Measurementgure 9: SLG46537V Resources Used	
	gure 10: Logic Analyzer – All Signals	
٠٠:	gs. c . ccg. c . u,c.	
T:	ables	
	able 1. Design Pinout	11
ı 2	IND THE BOTTO PINOUT	11



1 Terms and Definitions

ASIC Application specific integrated circuit

ASM Asynchronous state machine

CPLD Complex programmable logic device

ICs Integrated Circuits
MCU Microcontroller

2 References

For related documents and software, please visit:

GreenPAK™ Programmable Mixed-Signal Products | Renesas

Download our free GreenPAK Designer software [1] to open the .gp files [2] and view the proposed circuit design. Use the GreenPAK development tools [3] to freeze the design into your own customized IC in a matter of minutes. Renesas Electronics provides a complete library of application notes [4] featuring design examples, as well as explanations of features and blocks within the Renesas IC.

- [1] GreenPAK Designer Software, Software Download and User Guide, Renesas Electronics
- [2] AN-CM-280 Servo Demultiplexer.gp, GreenPAK Design File,

Renesas Electronics

- [3] GreenPAK Development Tools, GreenPAK Development Tools Webpage,
 - Renesas Electronics
- [4] GreenPAK Application Notes, GreenPAK Application Notes Webpage, Renesas Electronics



3 Introduction

Servo Motors are widely used for commercial and industrial applications as linear or rotary actuators. In this example the SG90 model is used, which is low cost, consumes little power, and is lightweight. This makes these type of servos ideal for consumer device RC toys such as RF-controlled race cars, airplanes, and others.

However, to properly control a servo motor, the electronic driver must generate appropriate voltage patterns to the servo motor DATA pin. The waveforms should be pulses shorter than 2 milliseconds, repeating every 20 milliseconds for one servo motor.

This application note will present the design of one 1 to 8 servo motor signal demultiplexer with the SLG46537V GreenPAK™ IC. The designed signal demultiplexer would drive up to 8 servo motors on 8 output pins with the multiplexed signal coming in on 1 input pin. The SLG46537V can also integrate additional functionality, such as additional logic or voltage monitoring, depending upon the system requirements.

The following sections will show:

- A servo motor 1 RF channel signal multiplex;
- The SLG46537V GreenPAK servo demultiplexer design in detail;
- How to drive 8 servo motors with 1 GreenPAK device.



Figure 1: SG90 Model Servo Motor



4 Servo Motor 1 RF Channel Multiplex

The standard for small 9g servo motors is that they operate from $0.5 \text{ ms} \sim 1.5 \text{ ms}$ HIGH pulses with a period of 20 milliseconds. 0.5 ms correlates to 0° , 1 ms to 90° , and 1.5 ms to 180° .

In this way, if we reserve a 2 milliseconds window for each motor pulse, 8 ms x 2 ms can be used for 8 motor pulse windows with the remaining 4 ms silence at the end used for synchronization. Figure 2 shows a time multiplex period of 20 ms for 8 motors, all at 90° position (1 ms pulses). Figure 3 shows a time multiplex period of 20 ms for 8 motors, all at 90° position (1 ms pulses) except for motor #5 at a 0° position (0.5 ms pulse).

Figure 2 and Figure 3 are waveforms of signed digital samples generated by a Python script for a sampling rate of 50,000 Hz.

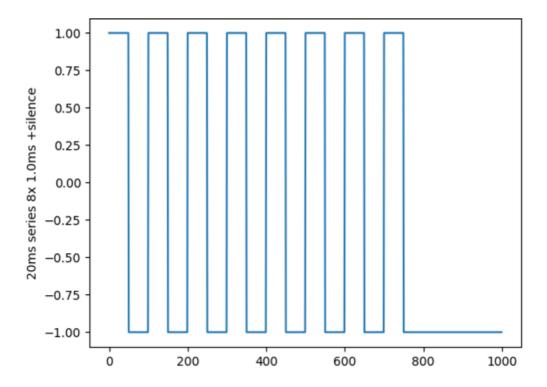


Figure 2: Time Multiplex - 8x 90° @ 50kS/s



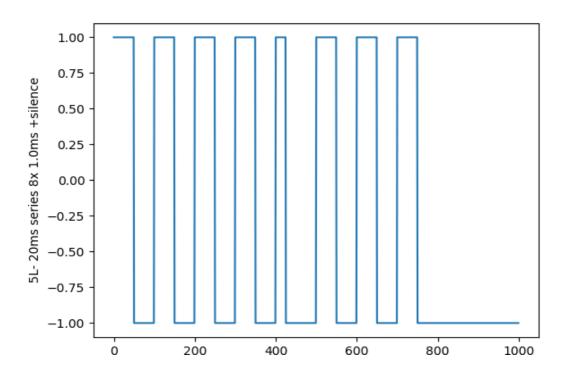


Figure 3: Time Multiplex – 7x 90°, #5 =0° @ 50kS/s



5 GreenPAK Design Schematic

The schematic of the GreenPAK design is shown in Figure 4. The fundamental blocks of the design are the internal Oscillator, 2x Counter, 2x Filter, 8x Flip-Flop, ASM with reset, 8x Pins with OE and Pull-downs, input pin and supply pins.

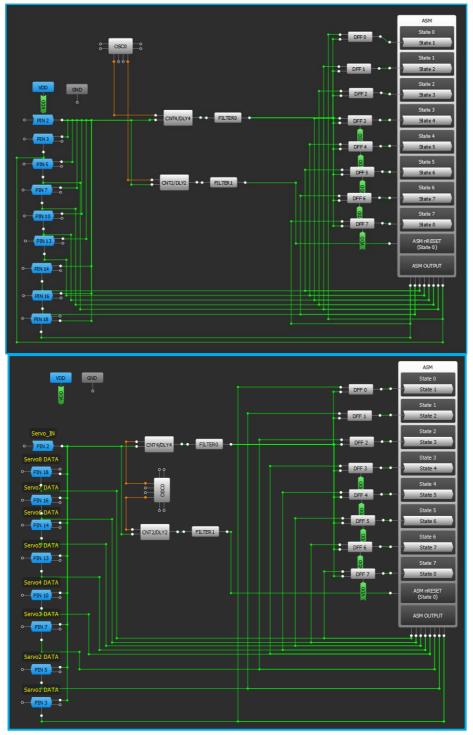


Figure 4: Top View of the GreenPAK Design Schematic



5.1 GreenPAK Timing Blocks

The OSC0 internal oscillator is used. It drives the CNT2 counter with 2 MHz/8/64 \approx 3.9 kHz and the CNT4 counter with 2 MHz/8/4 \approx 62.5 kHz. Settings are shown in Figure 5. CNT2 is set to trigger repeatedly on all falling edges (Delay Mode) and give a Non-inverted OUT after 4.096 ms. This is the 4 ms silence detection at the end of our 20 ms time multiplex period, which resets the ASM to State 0. CNT4 is set to trigger once every falling edge (One Shot Mode) after 96 μ s to give a short pulse to all Flip-Flop CLOCK inputs. Only the Flip-Flop of the current state has a HIGH input and will trigger the ASM to transition to the following state.



Figure 5: Close-up of Timing Blocks Settings

5.2 GreenPAK ASM

The Flip-Flops in the GreenPAK design are used to change the asynchronous state machine into a synchronous machine. As described in the previous section, CNT/DLY4 delivers a short pulse to all Flip-Flop CLOCK inputs, but only the Flip-Flop of the current state has a HIGH input and will trigger the transition to State +1. ASM runaway thru more than one state is prevented since all the other Flip-Flops were just loaded with LOW inputs, so the ASM has to wait until the next pulse for the next transition. This is necessary since all state transition conditions are the same 1 condition. Settings are shown in Figure 6.



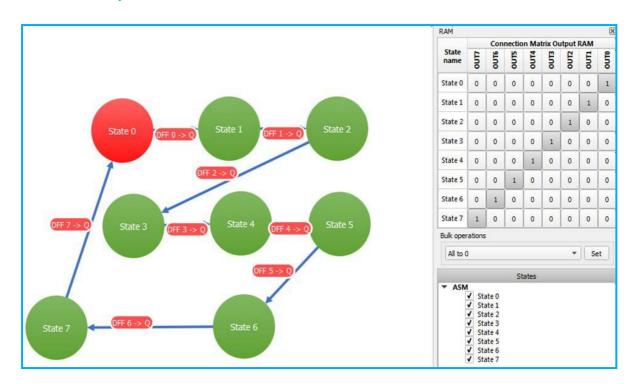


Figure 6: Close View of ASM Settings



6 GreenPAK Design Pinout

The Signal input IO0 is configured as a Digital in without Schmitt trigger. The ServoX DATA outputs are configured as 1x Push-Pull at OE = 1, at OE = 0 they are inputs with a 10 k Pull-down resistor. Pinout is shown in Table 1 and Figure 7.

Table 1: Design Pinout

Pin	Signal	Pin Function
#	Name	
1	V_{DD}	+5 V Supply
2	IO0	Signal Input
3	IO1	Servo1 DATA
4	IO2	
5	IO3	Servo2 DATA
6	104	
7	IO5	Servo3 DATA
8	106	
9	107	
10	IO8	Servo4 DATA
11	GND	Ground
12	IO9	
13	IO10	Servo5 DATA
14	IO11	Servo6 DATA
15	IO12	
16	IO13	Servo7 DATA
17	IO14	
18	IO15	Servo8 DATA
19	IO16	
20	IO17	

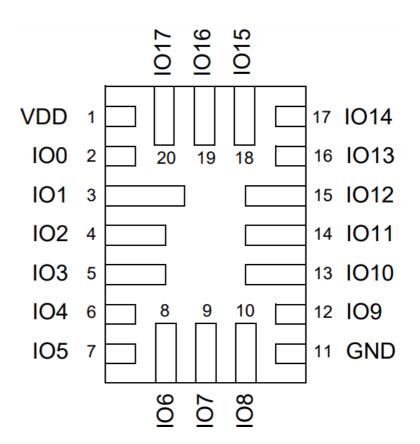


Figure 7: Pin Configuration - STQFN20L



7 Test Results

The Signal input is driven by an amplified Audio Out signal (0 ~ 5 V) generated by a Python script (Appendix A). Figure 8 shows the Signal Input in yellow and the Servo1 DATA output in blue. The generated .wav file has 20 seconds of choreographed servo movements and the GreenPAK design decodes all 8 ServoX DATA signals accordingly which is seen by movements of the servo motors.

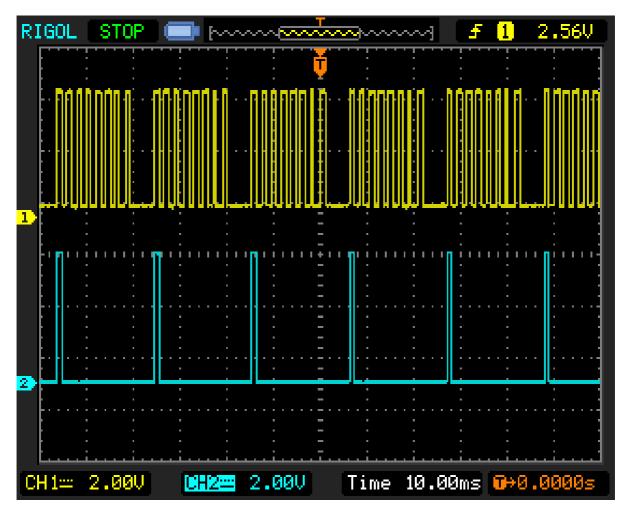


Figure 8: Input/Output - Measurement



8 Conclusion and Results Discussion

The Design of a Model Servo Motor Demultiplexer was presented. Through a GreenPAK design with the SLG46537V we have successfully implemented a lightweight, low-power, cost-effective solution. Figure 9 shows the resource usage of the SLG46537V. The design successfully decodes all 8 ServoX DATA signals from one Time Multiplexed signal input - Figure 10.

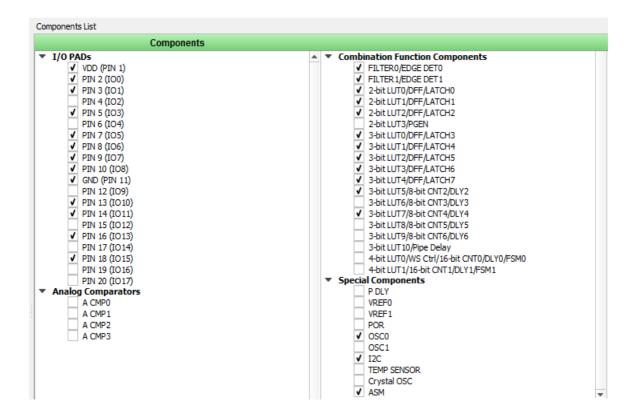


Figure 9: SLG46537V Resources Used

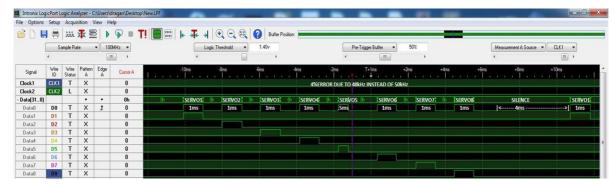


Figure 10: Logic Analyzer - All Signals



Appendix A Source Code

```
#servoMUX.py#################BEGIN#
import wave
import numpy as np
import matplotlib.pyplot as plt
def repeat48x(series):
               return np.concatenate(( series, series
ries, series, 
 ries, series, 
ries, series, series, series, series, series, series, series, series, series), axis=None)
 silence=-np.ones(200)
pulse10=np.concatenate((np.ones(50), -np.ones(50)), axis=None)
plt.plot(pulse10)
plt.ylabel('pulse 1.0ms')
plt.show()
pulse05=np.concatenate((np.ones(25), -np.ones(75)), axis=None)
plt.plot(pulse05)
plt.ylabel('pulse 0.5ms')
plt.show()
pulse15=np.concatenate((np.ones(75), -np.ones(25)), axis=None)
plt.plot(pulse15)
plt.ylabel('pulse 1.5ms')
plt.show()
series=np.concatenate((pulse10, pulse10, pulse10, pulse10, pulse10, pulse10, pulse10, pulse10, si-
lence), axis=None)
plt.plot(series)
plt.ylabel('20ms series 8x 1.0ms +silence')
plt.show()
second10=repeat48x(series)
plt.plot(second10)
plt.ylabel('1s- 20ms series 8x 1.0ms +silence')
 plt.show()
```



```
#second1L
series=np.concatenate((pulse05, pulse10, pulse10, pulse10, pulse10, pulse10, pulse10, pulse10, si-
lence), axis=None)
plt.plot(series)
plt.ylabel('1L- 20ms series 8x 1.0ms +silence')
plt.show()
second1L=repeat48x(series)
plt.plot(second1L)
plt.ylabel('1L-1s- 20ms series 8x 1.0ms +silence')
plt.show()
#second2L
series=np.concatenate((pulse10, pulse05, pulse10, pulse10, pulse10, pulse10, pulse10, pulse10, si-
lence), axis=None)
plt.plot(series)
plt.ylabel('2L- 20ms series 8x 1.0ms +silence')
plt.show()
second2L=repeat48x(series)
plt.plot(second2L)
plt.ylabel('2L-1s- 20ms series 8x 1.0ms +silence')
plt.show()
#second3L
series=np.concatenate((pulse10, pulse10, pulse10
lence), axis=None)
plt.plot(series)
plt.ylabel('3L- 20ms series 8x 1.0ms +silence')
plt.show()
second3L=repeat48x(series)
plt.plot(second3L)
plt.ylabel('3L-1s- 20ms series 8x 1.0ms +silence')
plt.show()
#second4L
series=np.concatenate((pulse10, pulse10, pulse10, pulse05, pulse10, pulse10, pulse10, pulse10, si-
lence), axis=None)
plt.plot(series)
plt.ylabel('4L- 20ms series 8x 1.0ms +silence')
plt.show()
second4L=repeat48x(series)
```



```
plt.plot(second4L)
plt.ylabel('4L-1s- 20ms series 8x 1.0ms +silence')
plt.show()
#second5L
series=np.concatenate((pulse10, pulse10, pulse10, pulse10, pulse05, pulse10, pulse10, pulse10, si-
lence), axis=None)
plt.plot(series)
plt.ylabel('5L- 20ms series 8x 1.0ms +silence')
plt.show()
second5L=repeat48x(series)
plt.plot(second5L)
plt.ylabel('5L-1s- 20ms series 8x 1.0ms +silence')
plt.show()
#second6L
series=np.concatenate((pulse10, pulse10, pulse10, pulse10, pulse10, pulse10, pulse05, pulse10, pulse10, si-
lence), axis=None)
plt.plot(series)
plt.ylabel('6L- 20ms series 8x 1.0ms +silence')
plt.show()
second6L=repeat48x(series)
plt.plot(second6L)
plt.ylabel('6L-1s- 20ms series 8x 1.0ms +silence')
plt.show()
#second7L
series=np.concatenate((pulse10, pulse10, pulse10, pulse10, pulse10, pulse10, pulse10, pulse10, si-
lence), axis=None)
plt.plot(series)
plt.ylabel('7L- 20ms series 8x 1.0ms +silence')
plt.show()
second7L=repeat48x(series)
plt.plot(second7L)
plt.ylabel('7L-1s- 20ms series 8x 1.0ms +silence')
plt.show()
#second8L
series=np.concatenate((pulse10, pulse10, pulse10
lence), axis=None)
plt.plot(series)
```



```
plt.ylabel('8L- 20ms series 8x 1.0ms +silence')
plt.show()
second8L=repeat48x(series)
plt.plot(second8L)
plt.ylabel('8L-1s- 20ms series 8x 1.0ms +silence')
plt.show()
w=wave.open("servo.wav", 'wb')
w.setnchannels(1)
w.setsampwidth(1)
w.setframerate(48000)
#w.setnframes(24000)
#w.setcomptype('NONE', 'wav')
w.writeframesraw(100*second10.astype(np.int8))
w.writeframesraw(100*second10.astype(np.int8))
w.writeframesraw(100*second10.astype(np.int8))
w.writeframesraw(100*second10.astype(np.int8))
w.writeframesraw(100*second1L.astype(np.int8))
w.writeframesraw(100*second2L.astype(np.int8))
w.writeframesraw(100*second3L.astype(np.int8))
w.writeframesraw(100*second4L.astype(np.int8))
w.writeframesraw(100*second5L.astype(np.int8))
w.writeframesraw(100*second6L.astype(np.int8))
w.writeframesraw(100*second7L.astype(np.int8))
w.writeframesraw(100*second8L.astype(np.int8))
w.writeframesraw(100*second10.astype(np.int8))
w.writeframesraw(100*second10.astype(np.int8))
w.writeframesraw(100*second10.astype(np.int8))
w.writeframesraw(100*second10.astype(np.int8))
w.close()
#servoMUX.py#################END#
```



Revision History

Revision	Date	Description
1.0	17-May-2019	Initial Version

IMPORTANT NOTICE AND DISCLAIMER

RENESAS ELECTRONICS CORPORATION AND ITS SUBSIDIARIES ("RENESAS") PROVIDES TECHNICAL SPECIFICATIONS AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS OR IMPLIED, INCLUDING, WITHOUT LIMITATION, ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for developers skilled in the art designing with Renesas products. You are solely responsible for (1) selecting the appropriate products for your application, (2) designing, validating, and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. Renesas grants you permission to use these resources only for development of an application that uses Renesas products. Other reproduction or use of these resources is strictly prohibited. No license is granted to any other Renesas intellectual property or to any third party intellectual property. Renesas disclaims responsibility for, and you will fully indemnify Renesas and its representatives against, any claims, damages, costs, losses, or liabilities arising out of your use of these resources. Renesas' products are provided only subject to Renesas' Terms and Conditions of Sale or other applicable terms agreed to in writing. No use o any Renesas resources expands or otherwise alters any applicable warranties or warranty disclaimers for these products.

(Disclaimer Rev.1.0 Mar 2020)

Corporate Headquarters

TOYOSU FORESIA, 3-2-24 Toyosu, Koto-ku, Tokyo 135-0061, Japan www.renesas.com

Trademarks

Renesas and the Renesas logo are trademarks of Renesas Electronics Corporation. All trademarks and registered trademarks are the property of their respective owners.

Contact Information

For further information on a product, technology, the most up-to-date version of a document, or your nearest sales office, please visit:

www.renesas.com/contact/

IMPORTANT NOTICE AND DISCLAIMER

RENESAS ELECTRONICS CORPORATION AND ITS SUBSIDIARIES ("RENESAS") PROVIDES TECHNICAL SPECIFICATIONS AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS OR IMPLIED, INCLUDING, WITHOUT LIMITATION, ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, OR NON-INFRINGEMENT OF THIRD-PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for developers who are designing with Renesas products. You are solely responsible for (1) selecting the appropriate products for your application, (2) designing, validating, and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. Renesas grants you permission to use these resources only to develop an application that uses Renesas products. Other reproduction or use of these resources is strictly prohibited. No license is granted to any other Renesas intellectual property or to any third-party intellectual property. Renesas disclaims responsibility for, and you will fully indemnify Renesas and its representatives against, any claims, damages, costs, losses, or liabilities arising from your use of these resources. Renesas' products are provided only subject to Renesas' Terms and Conditions of Sale or other applicable terms agreed to in writing. No use of any Renesas resources expands or otherwise alters any applicable warranties or warranty disclaimers for these products.

(Disclaimer Rev.1.01)

Corporate Headquarters

TOYOSU FORESIA, 3-2-24 Toyosu, Koto-ku, Tokyo 135-0061, Japan www.renesas.com

Trademarks

Renesas and the Renesas logo are trademarks of Renesas Electronics Corporation. All trademarks and registered trademarks are the property of their respective owners.

Contact Information

For further information on a product, technology, the most up-to-date version of a document, or your nearest sales office, please visit www.renesas.com/contact-us/.