

IGBT

Usage Notes on Gate Drive

Introduction

This document provides notes on gate drive conditions for Renesas IGBT and FRD products.

Contents

1. IGBT DRIVE GATE VOLTAGE	2
1.1 Recommended gate voltage	2
1.2 VCE(sat), short-circuit withstand time (SCWT)	2
2. DRIVE CURRENT	3
3. SELECTING GATE RESISTOR Rg	4
3.1 External gate resistor Rg selection	4
3.2 Turn on/Turn off Rg selection	4
3.3 Switching time	4
3.3.1 Switching time (in relation to Rg)	4
3.3.2 Switching time (comparison of process generations)	6
3.3.3 Switching time (dead time)	7
3.4 Switching loss	8
3.5 Surge voltage	9
3.5.1 Surge voltage (turn off)	9
3.5.2 Surge voltage (FRD recovery operation)	9
3.6 False turn on	10
3.7 Ringing	11
3.7.1 Ringing and other noise (parasitic component)	11
3.7.2 Ringing (FRD recovery operation during low current)	12
Revision History	18

1. IGBT DRIVE GATE VOLTAGE

1.1 Recommended gate voltage

Figure 1-1 shows output characteristics of the Renesas JP6831JWS IGBT.

The recommended gate voltage when the IGBT is on is $V_{GE} = 15\text{ V}$.

The effect of gate voltage on operations is as follows.

- When V_{GE} is low:
Stress resulting from increased loss may damage the device.
- When V_{GE} is high:
 $V_{CE(sat)}$ decreases, resulting in less loss, but short-circuit withstand time (SCWT) decreases and there is greater probability of device damage in the event of a short circuit.
Surges may cause over-rating, another cause of damage to the device.

The absolute maximum V_{GES} rating is noted on each product datasheet;

always use IGBT within the rating range.

*Exceeding maximum rating may destroy gate oxide film and cause malfunction.

Off-state gate voltage should be set to a negative value (-5 V to -10 V) to prevent false turn on during upper and lower arm operation.

 


Figure 1-1 $V_{CE} - I_C$ characteristics (AE4 RJP6831JWS)

1.2 $V_{CE(sat)}$, short-circuit withstand time (SCWT)

Increasing gate voltage lowers $V_{CE(sat)}$, but also decreases withstand time (t_{sc}) at load short circuit (arm short circuit), as shown in Figure 1-2.

Gate drive voltage must be determined based on the relationship between $V_{CE(sat)}$ and t_{sc} .

Choose the optimum point for your application.

 


Figure 1-2 tsc - VCE(sat) (AE4 RJP6831JWS)

2. DRIVE CURRENT

Gate current I_g flows because the gate is charged or discharged during IGBT turn-on and turn-off.

If I_g is not sufficiently large, switching speed decreases, and may incur increased loss.

To maximize IGBT switching performance, design the driver circuit with a current capacity sufficient for the I_g (peak) shown below.

* When calculating I_g , it is necessary to consider chip built-in resistor r_g and internal resistor R_S of the driver circuit (Figure 2-1).

$$I_g(\text{peak}) = \frac{V_{GE(\text{on})} - V_{GE(\text{off})}}{(R_S + R_g + r_g)_{\text{min}}}$$

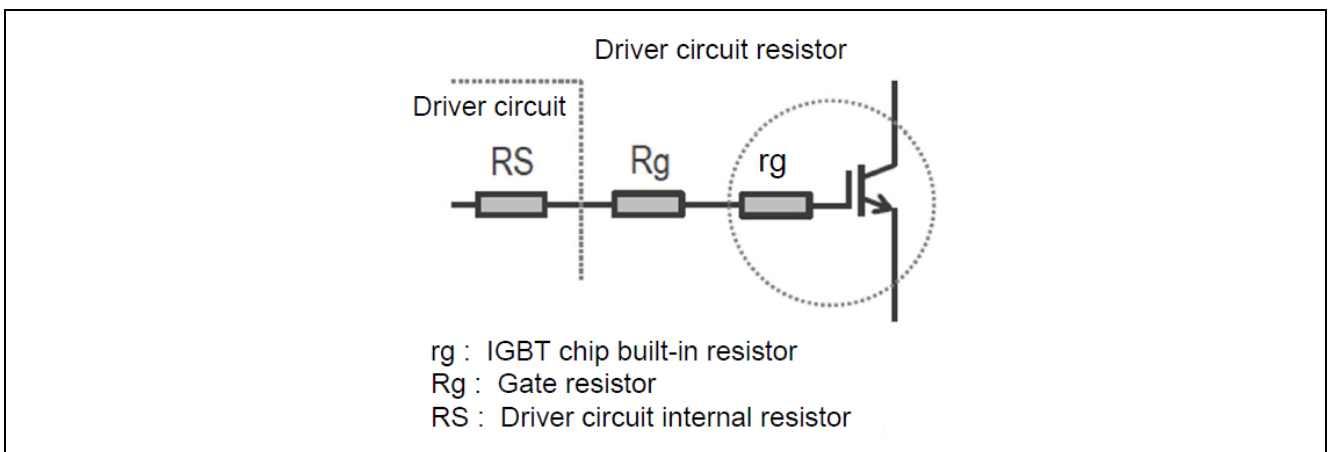


Figure 2-1 Gate Resistors

3. SELECTING GATE RESISTOR Rg

3.1 External gate resistor Rg selection

Gate resistor Rg should be optimally set to enable the most efficient product handling.

As shown in Figure 3-1, the external Rg value may impact characteristics.

--- Better,
 --- Worse

	Switching time	Switching loss	Surge voltage	False turn on	Ringing noise
Small Rg	↘	↘	↗	↗	↗
Big Rg	↗	↗	↘	↘	↘

Figure 3-1 Impact of gate resistance on key characteristics

As indicated above, when selecting Rg, consider the entire configuration, including switching time, switching loss, surge voltage and ringing, as well as the EMI noise of the entire system.

3.2 Turn on/Turn off Rg selection

Although Rg is generally indicated as shown in Figure 3-2(a) below, the product can be used more efficiently by setting two resistors in series, Rg on and Rg off for IGBT turn-on/turn-off, as shown in Figure 3-2(b).

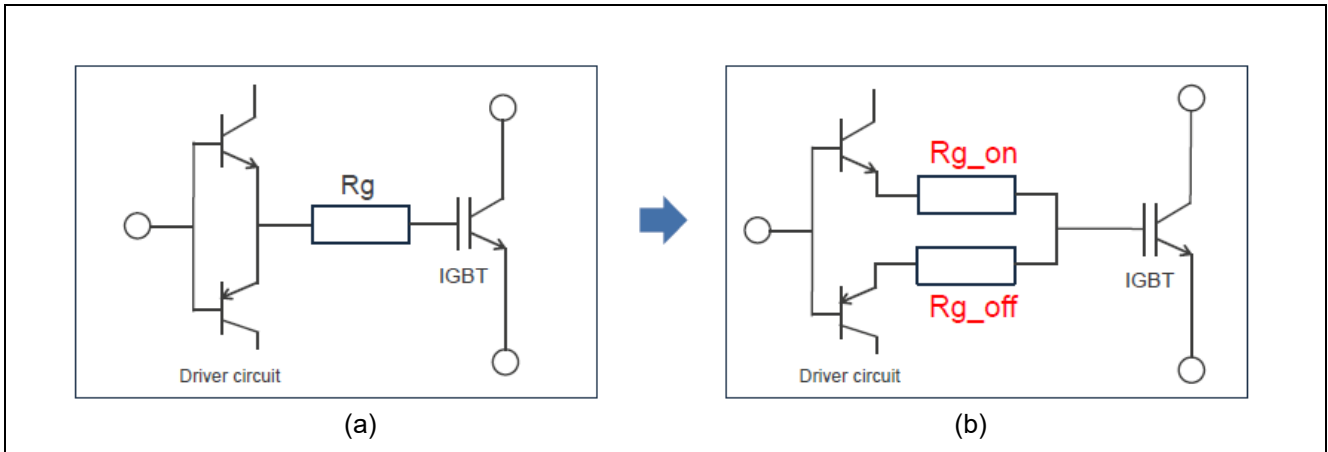


Figure 3-2 Gate resistor Rg on and Rg off

3.3 Switching time

3.3.1 Switching time (in relation to Rg)

As shown in Figure 3-3, switching time increases as Rg increases, and decreases as Rg decreases.

 


Figure 3-3 Rg vs. switching times (AE4 RJP6831JWS)

Figure 3-4 shows the difference in the waveforms of VGE, VCE, and IC during switching operation at Rg = 2, 10 ohm.

 


Figure 3-4 VGE, VCE, and IC waveforms during AE4 RJP6831 JWS SW operation

3.3.2 Switching time (comparison of process generations)

Differing IGBT process generations may have considerably different switching characteristics even within the same rating class. The latest-generation Renesas IGBT AE5 for automotive use has a smaller cell size than the current AE4 to reduce conduction loss.

AE5 therefore has higher gate capacitance and slower speed for the same gate resistance (Figure 3-5(a), (b)). A smaller R_g drive is required to achieve the same switching speed as AE4. (Figure 3-5(c))

When considering products of differing process generations, optimize drive conditions such as gate resistance according to the switching characteristics of each product.

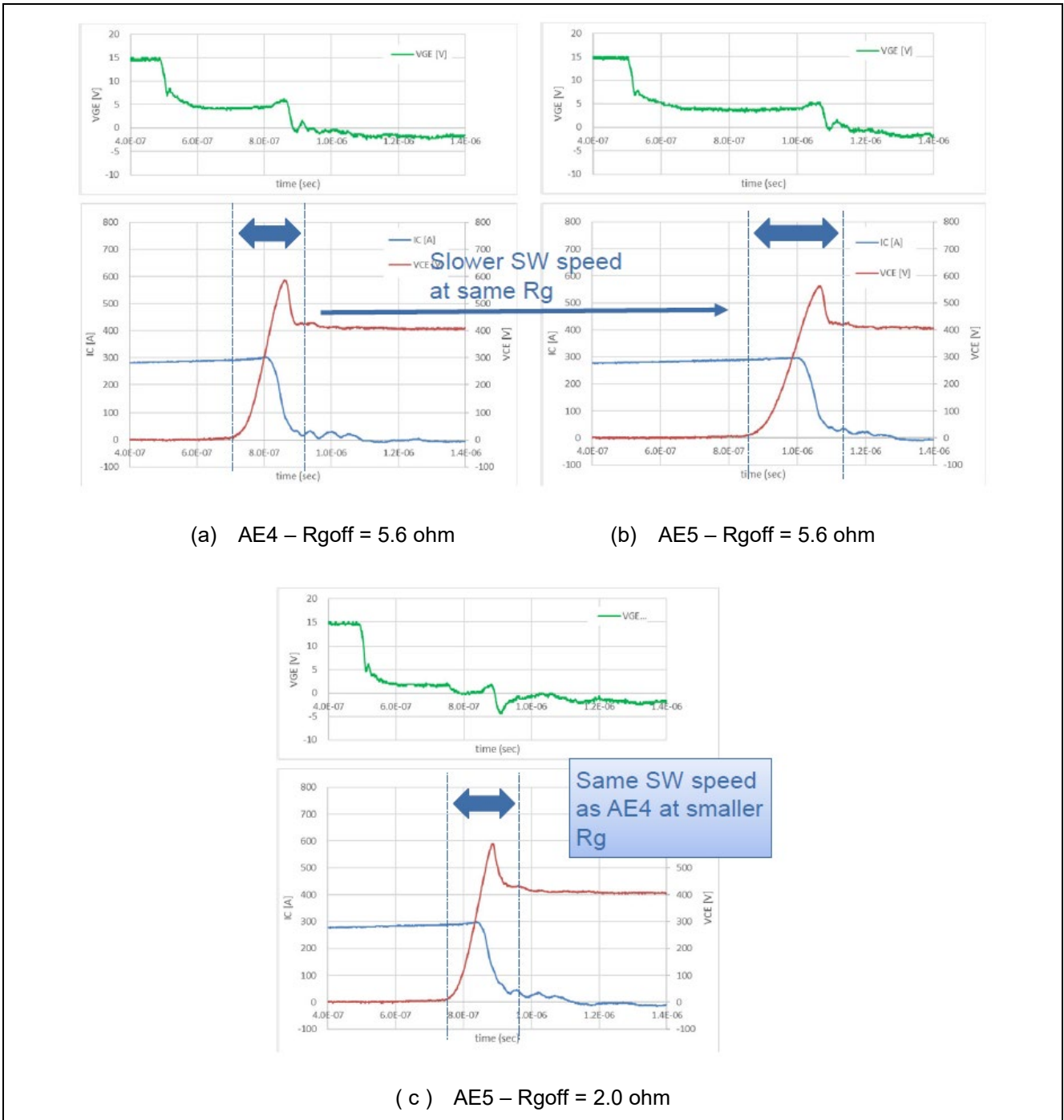


Figure 3-5 Renesas AE4/AE5 turn-off waveform comparison

3.3.3 Switching time (dead time)

As shown in Figure 3-6, a dead time must be set for the on/off switching timing in inverter circuits to prevent a short circuit between the upper and lower arms.

The dead time should generally be set for longer than the IGBT switching time.

Consideration should be given to R_g and other gate drive conditions, as well as temperature characteristics and other factors which may impact switching time.

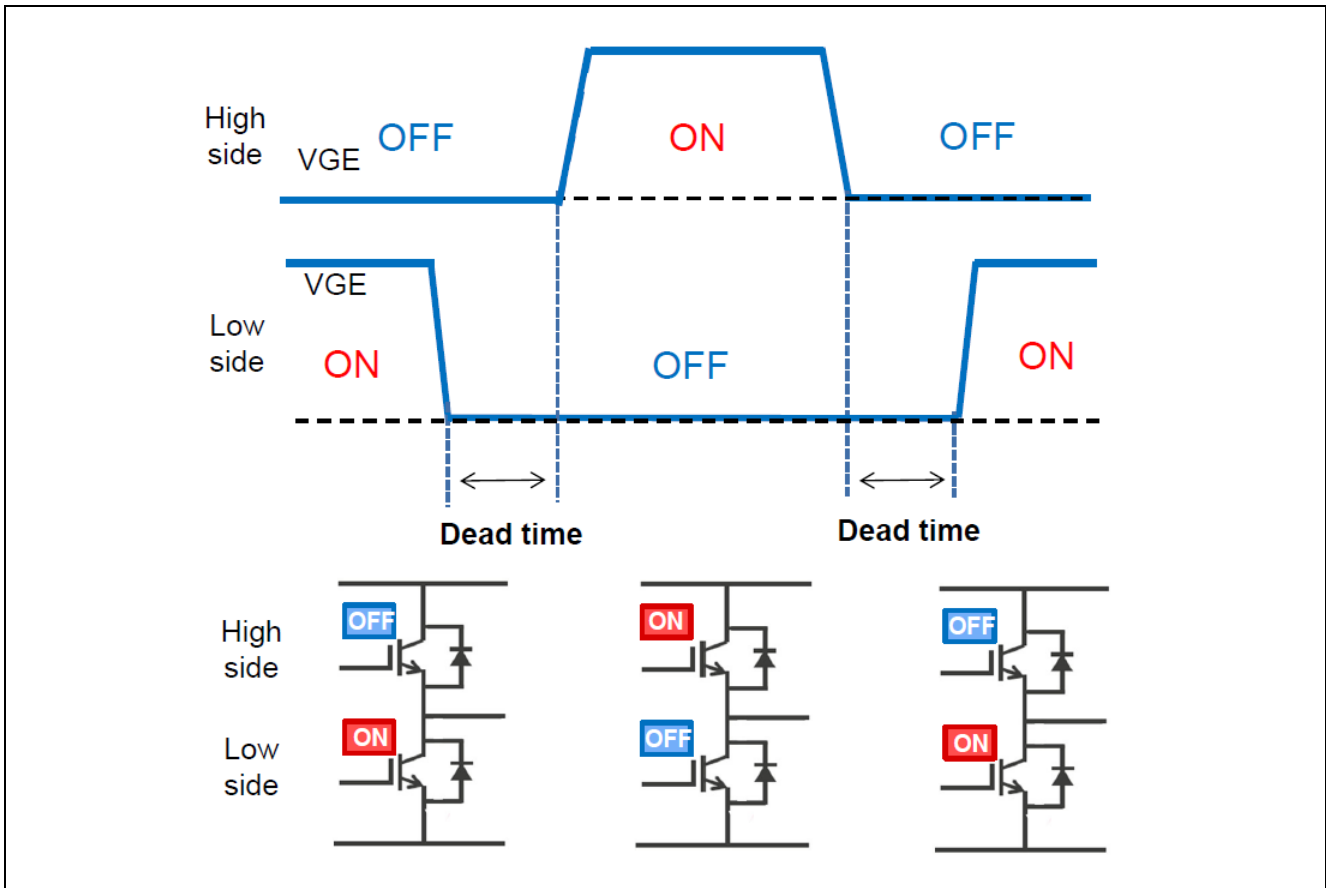


Figure 3-6 Upper/lower arm operation timing chart

Be careful with dead time settings when increasing the R_g value.

As shown on pp. 4-5, increasing R_{g_on} also increases $t_d(on)$ and t_r ; similarly, increasing R_{g_off} increases $t_d(off)$ and t_f .

As shown in Figure 3-7, extended switching time may cause an overlap between the ON time of the upper/lower arms, resulting in a short circuit between the two arms.

In the worst case, the heat produced by the short circuit current may damage the product. Therefore, set a generous dead time t to prevent short circuits. Also, carefully consider $t_d(off)$, because it is greater than $t_d(on)$, t_r , and t_f , and it has a high dependence on R_g (Figure 3-3).

While keeping the above in mind, make sure you set the most appropriate margin, as a long dead time will decrease efficiency and limit operating frequency.

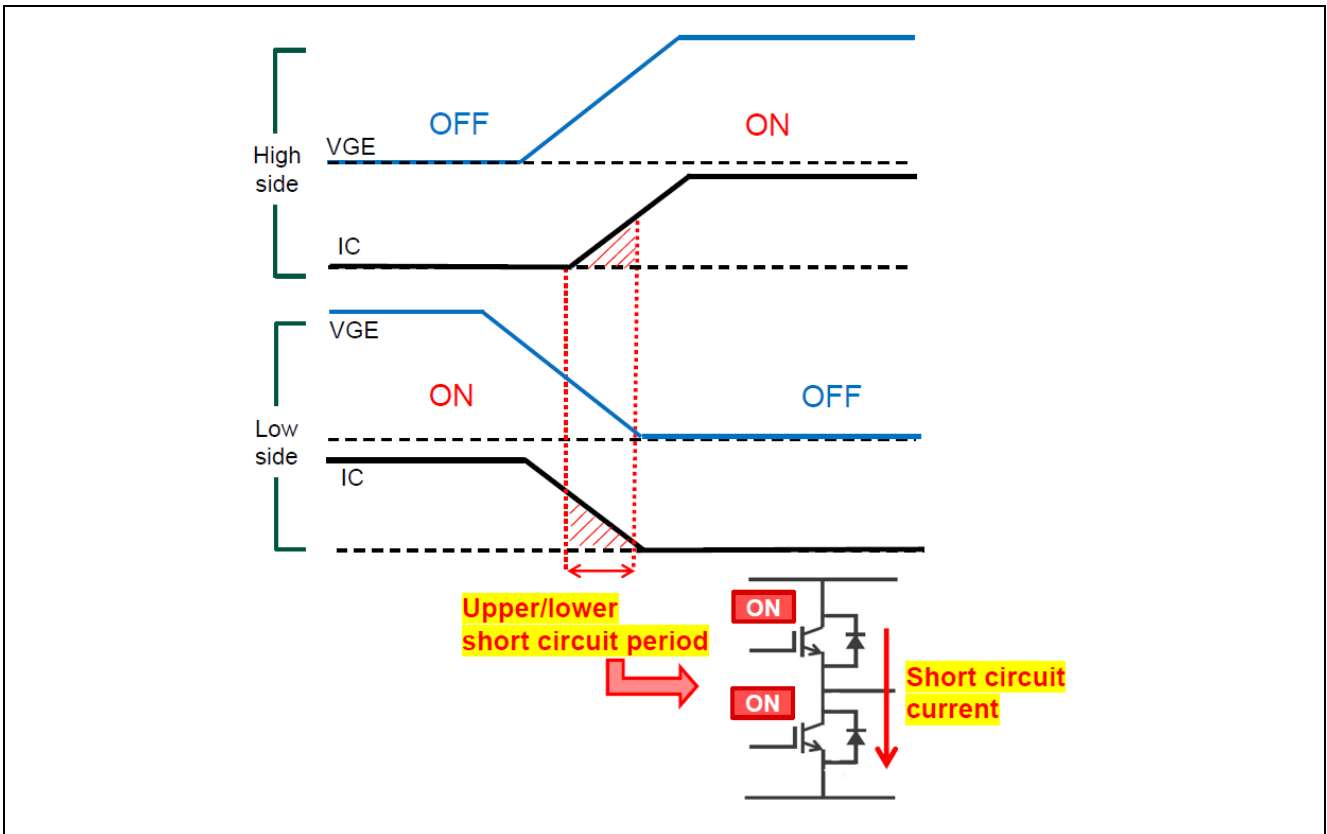


Figure 3-7 Upper/lower short circuit waveform example

3.4 Switching loss

Figure 3-8 shows the relationship between R_g and switching loss.

Increasing gate resistance normally extends switching time and increases switching loss.

Selecting low gate resistance speeds up switching time and reduces switching loss, but surges and ringing generated by di/dt and dv/dt may cause problems due to product damage and malfunctions, noise.

When selecting R_g , consider the trade-off between switching loss and surges, ringing.

Careful selections are advised.

 


Figure 3-8 Relationship between E_{on}/E_{off} and R_g (AE4 RJP6831JWS)

3.5 Surge voltage

3.5.1 Surge voltage (turn off)

Surge voltage generated at turn-off depends on the collector current di/dt value as shown in Figure 3-9.

As mentioned earlier, decreasing Rg_off reduces Eoff, but causes off-surge voltage to increase as the di/dt value increases.

Figure 3-10 shows the relationship between off-surge voltage and Eoff. This relationship causes a tradeoff between surge and Eoff in Renesas AE4 products.

Make sure turn-off surge voltage does not exceed rated voltage. At the same time, consider the effect on loss when adjusting Rg_off.

 


Figure 3-9 Rg vs. di/dt (AE4 RJP6831JWS)

 


Figure 3-10 Eoff vs. surge (AE4 RJP6831JWS)

3.5.2 Surge voltage (FRD recovery operation)

The recovery current produced by the FRD recovery operation (Figure 3-11) generates a recovery surge at Vak.

As shown in Figure 3-12, there is a proportional relationship between di/dt and the recovery current.

A steep di/dt may generate a surge which exceeds the rating and increases the chance of damage to the device.

Rg should therefore be adjusted with due consideration to the effect on loss.

 


Figure 3-11 FRD waveform during recovery operation

 


Figure 3-12 Relationship between di/dt and recovery current

3.6 False turn on

As shown in Figure 3-13, when IGBT1 is turned on, the IGBT2 Vce rises rapidly. The IGBT2 Cgc yields a displacement current *i* from the collector to the gate.

$$i = C_{gc} \times dv/dt$$

Current *i* pushes up Vge through gate resistor Rg2, and if dv/dt is steep, it generates a surge in Vge (Figure 3-14).

If the surge exceeds Vge(off), a false ignition occurs at IGBT2.

This can be prevented by setting IGBT off voltage to a negative value (-5 to -10V) as described on p. 2, which will increase Rg.

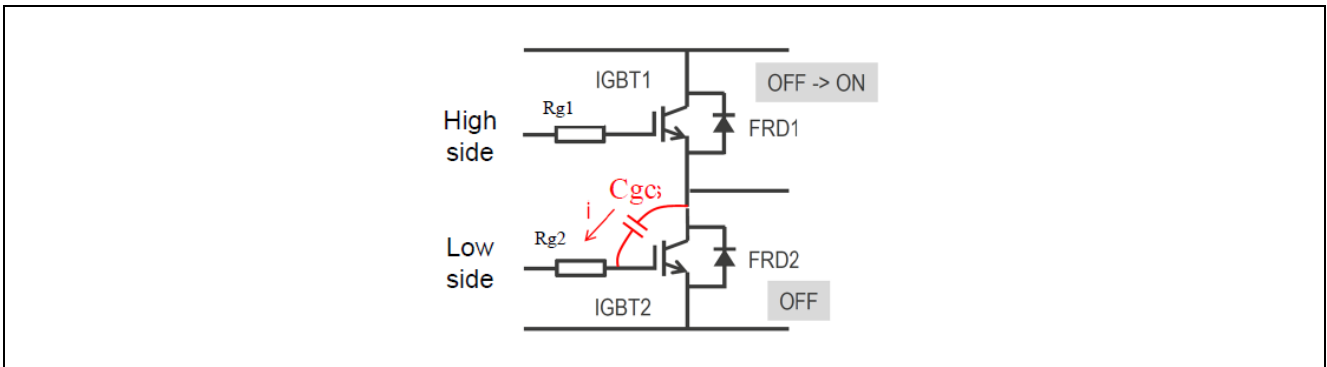


Figure 3-13 Parasitic capacitance during upper/lower arm operation

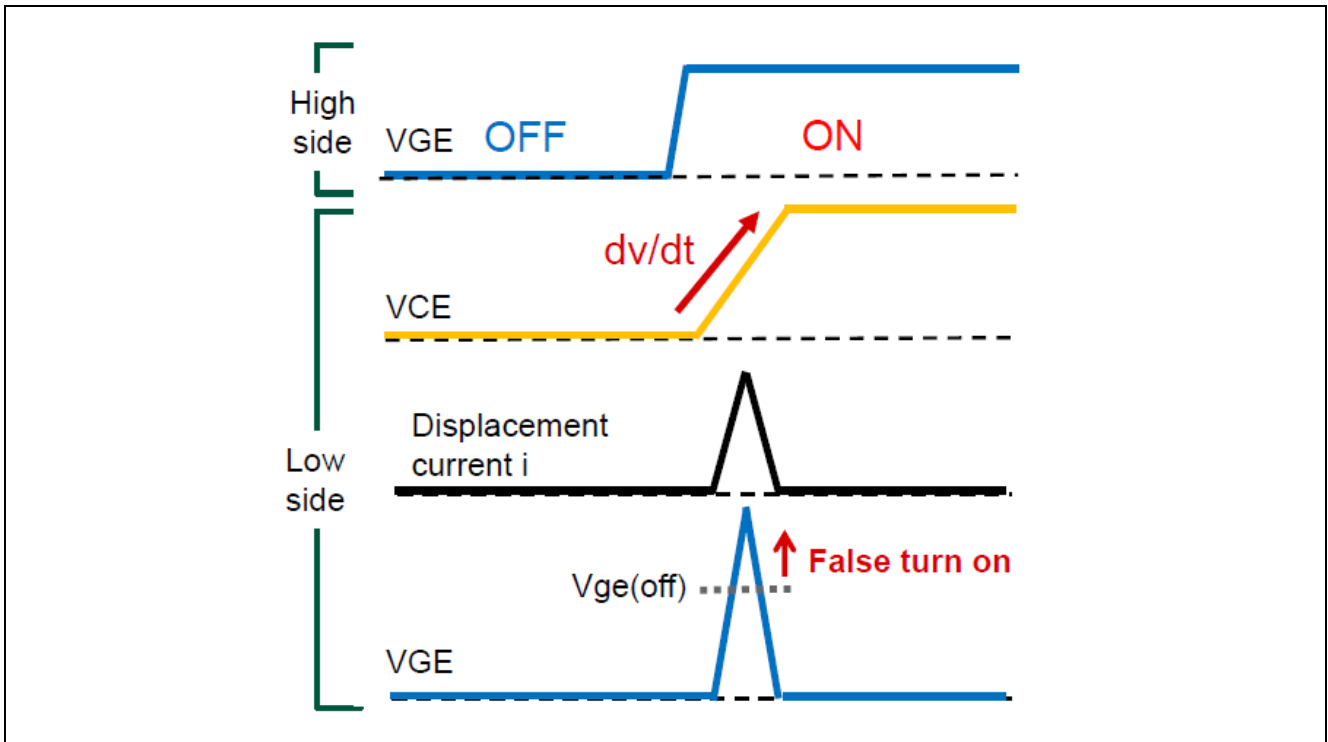


Figure 3-14 Surges during upper/lower arm operation

3.7 Ringing

3.7.1 Ringing and other noise (parasitic component)

Noise such as ringing may occur during switching if wiring inductance and other parasitic components of an IGBT circuit are high.

Ringing may be suppressed by increasing gate resistance.

In paralleled usage, suppress ringing by connecting individual gate resistors.

Click [Usage Notes for Paralleled IGBT](#) for more information.

Renesas offers a lineup of anti-ringing products with the built-in r_g shown in Figure 3-15.

See individual product data sheets for more details.

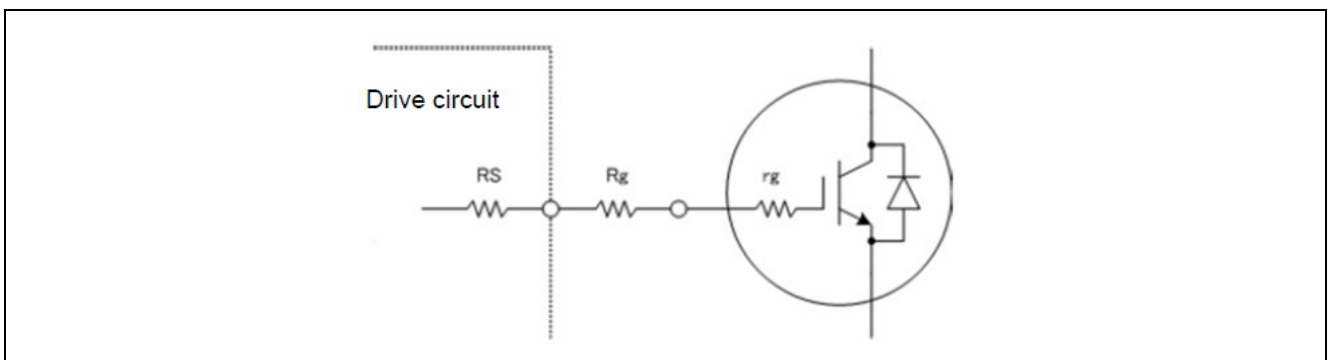


Figure 3-15 Drive circuit resistance components

3.7.2 Ringing (FRD recovery operation during low current)

Figure 3-16 shows low-current recovery waveforms for competitor products. In the FRD recovery operation at low current, the recovery current tends to decrease faster, while the simultaneous steep surge voltage may cause ringing.

Ringing can be suppressed by increasing R_g . Renesas AE4 and AE5 FRDs boast an advantage here, as R_{g_on} can be suppressed to a smaller value than that of competitor products. (Figure 3-17)

Ultimately, R_g must be set based on EMI noise considerations.

 


Figure 3-16 Low-current recovery surge for competitor products

 


Figure 3-17 Low-current recovery surge for AE4 and AE5 FRDs

Appendix: Definitions

Gate charge

Like MOSFETs, IGBTs have a parasitic capacitance component.

The capacitance component shown in Figure 4-1 is an important parameter determining drive current and driver circuit power loss.

- **Q_{ge} charge period**
Q_{ge} is required to charge V_{GE} (C_{ge}), which is required for the collector current to flow.
Q_{gc} charge period
Q_{gc} is required to charge C_{gc}. During this period, the Miller effect causes the apparent capacitance to increase, while V_{GE} change appears flat.
V_{CE} decreases to V_{CE(sat)} during this period.
- **Q_g charge period**
Q_g is the ultimate amount of charge required to bring V_{GE} to 15V.
It is the amount of charge required to turn on the IGBT completely.

 


Figure 4-1 Target parasitic capacitance

 


Figure 4-2 Relationship of gate charge and V_{GE}/V_{CE}

Switching characteristics

IGBTs are used as switches in power conversion.

Switching characteristics are measured using the switching characteristic measurement circuit shown in Figure 4-3.

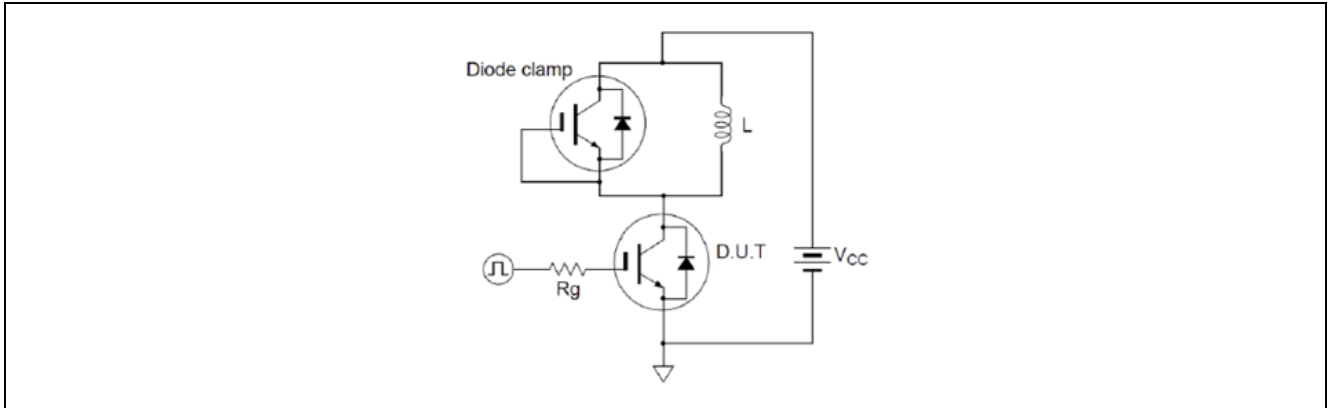


Figure 4-3 Switching characteristic measurement circuit

Important parameters in switching characteristics are described on the following page.

Switching characteristics (switching time)

- $t_d(\text{on})$: turn-on delay time
Time for the gate-emitter voltage to rise from 10% of the forward-bias voltage to 10% of the Collector current
- t_r : rise time
Time for the collector current to rise from 10% to 90%
- $t_d(\text{off})$: turn-off delay time
Time for the gate-emitter voltage to fall from 90% of the forward-bias voltage to 90% of the collector current
- t_f : fall time
Time for collector current to fall from 90% to 10%

 


Figure 4-4 Switching waveforms

Switching characteristics (switching loss)

Switching loss is shown in Figure 4-6.

Off-period loss can be calculated as $V_{CE} \times I_C$.

Calculating IGBT loss is extremely important for estimating the application's power consumption and junction temperature T_j .

Turn-on loss energy	E_{on}	Integral value of collector loss that occurs from the start of turn-on until the collector-emitter voltage reaches the specified value
Turn-off loss energy	E_{off}	Integral value of collector loss that occurs from the start of turn-off until the collector-emitter voltage reaches the specified value
Switching loss energy	E_{total}	Sum of E_{on} and E_{off}

Figure 4-5 Definition of switching loss terms

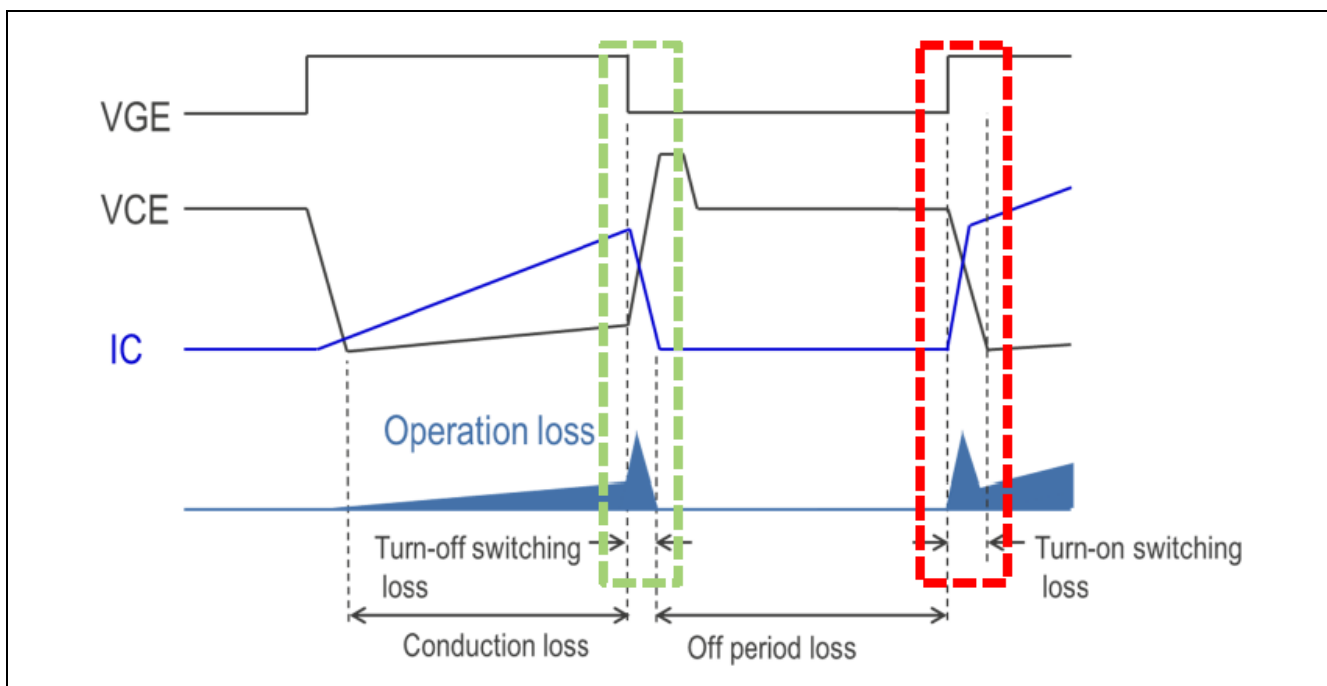


Figure 4-6 Switching loss

di/dt and surge voltage

di/dt refer to the change in current during the switching transition period.

The recovery current converges rapidly during FRD operation, while the steep di/dt causes a surge voltage at the parasitic inductance.

$$V_{surge} = L \times di/dt$$

The surge voltage caused by high voltage and high current is considerable, a key point as this can cause damage to the product if the rated value is exceeded.

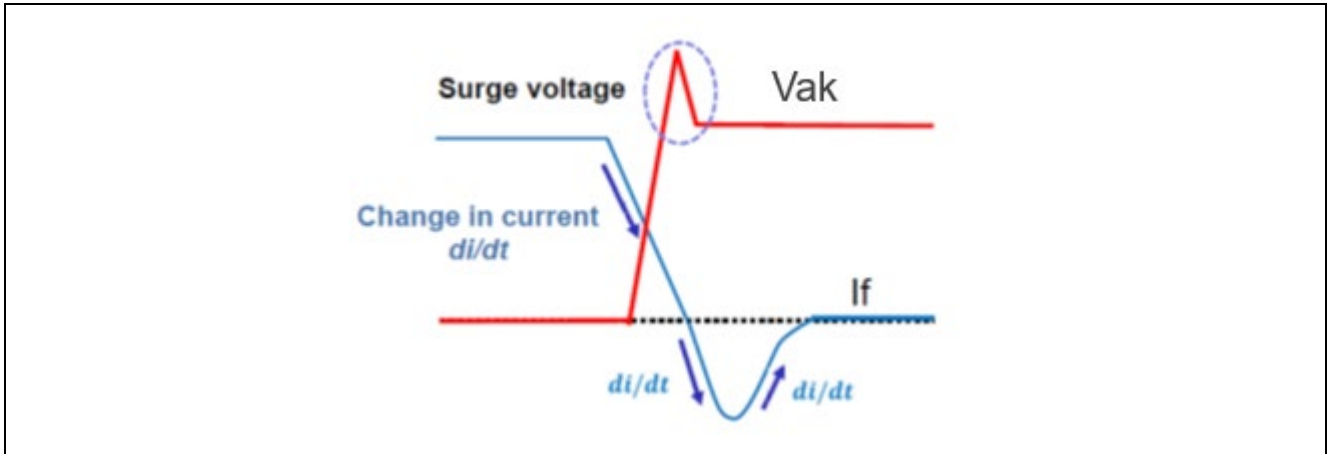


Figure 4-7 Surge voltage and di/dt

Ringing

As shown in Figure 4-8, ringing is the phenomenon in which the waveform oscillates compared to the ideal waveform.

While ringing may be caused by several factors, this document focuses on two factors: parasitic components and FRD recovery operation.

- Ringing caused by parasitic components
Ringing can be caused by parasitic components such as parasitic inductance of conductors and the parasitic capacitance of IGBTs (Figure 4-9). Designing the wiring as short as possible is an essential countermeasure. Click [Usage Notes for Paralleled IGBT](#) for more information on ringing (gate oscillation) in paralleled operation.
- Ringing caused by FRD recovery operation at low current
Ringing occurs due to steep current convergence caused by the recovery current during FRD recovery operation at low current (Figure 4-10).

 


Figure 4-8 Ringing

 


Figure 4-9 Circuit parasitic components

 


Figure 4-10 Ringing caused by recovery current at low current

Revision History

Rev.	Date	Description	
		Page	Summary
1.00	2024/10/01	-	First edition

Notice

1. Descriptions of circuits, software and other related information in this document are provided only to illustrate the operation of semiconductor products and application examples. You are fully responsible for the incorporation or any other use of the circuits, software, and information in the design of your product or system. Renesas Electronics disclaims any and all liability for any losses and damages incurred by you or third parties arising from the use of these circuits, software, or information.
2. Renesas Electronics hereby expressly disclaims any warranties against and liability for infringement or any other claims involving patents, copyrights, or other intellectual property rights of third parties, by or arising from the use of Renesas Electronics products or technical information described in this document, including but not limited to, the product data, drawings, charts, programs, algorithms, and application examples.
3. No license, express, implied or otherwise, is granted hereby under any patents, copyrights or other intellectual property rights of Renesas Electronics or others.
4. You shall be responsible for determining what licenses are required from any third parties, and obtaining such licenses for the lawful import, export, manufacture, sales, utilization, distribution or other disposal of any products incorporating Renesas Electronics products, if required.
5. You shall not alter, modify, copy, or reverse engineer any Renesas Electronics product, whether in whole or in part. Renesas Electronics disclaims any and all liability for any losses or damages incurred by you or third parties arising from such alteration, modification, copying or reverse engineering.
6. Renesas Electronics products are classified according to the following two quality grades: "Standard" and "High Quality". The intended applications for each Renesas Electronics product depends on the product's quality grade, as indicated below.

"Standard": Computers; office equipment; communications equipment; test and measurement equipment; audio and visual equipment; home electronic appliances; machine tools; personal electronic equipment; industrial robots; etc.

"High Quality": Transportation equipment (automobiles, trains, ships, etc.); traffic control (traffic lights); large-scale communication equipment; key financial terminal systems; safety control equipment; etc.

Unless expressly designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not intended or authorized for use in products or systems that may pose a direct threat to human life or bodily injury (artificial life support devices or systems; surgical implantations; etc.), or may cause serious property damage (space system; undersea repeaters; nuclear power control systems; aircraft control systems; key plant systems; military equipment; etc.). Renesas Electronics disclaims any and all liability for any damages or losses incurred by you or any third parties arising from the use of any Renesas Electronics product that is inconsistent with any Renesas Electronics data sheet, user's manual or other Renesas Electronics document.
7. No semiconductor product is absolutely secure. Notwithstanding any security measures or features that may be implemented in Renesas Electronics hardware or software products, Renesas Electronics shall have absolutely no liability arising out of any vulnerability or security breach, including but not limited to any unauthorized access to or use of a Renesas Electronics product or a system that uses a Renesas Electronics product. RENESAS ELECTRONICS DOES NOT WARRANT OR GUARANTEE THAT RENESAS ELECTRONICS PRODUCTS, OR ANY SYSTEMS CREATED USING RENESAS ELECTRONICS PRODUCTS WILL BE INVULNERABLE OR FREE FROM CORRUPTION, ATTACK, VIRUSES, INTERFERENCE, HACKING, DATA LOSS OR THEFT, OR OTHER SECURITY INTRUSION ("Vulnerability Issues"). RENESAS ELECTRONICS DISCLAIMS ANY AND ALL RESPONSIBILITY OR LIABILITY ARISING FROM OR RELATED TO ANY VULNERABILITY ISSUES. FURTHERMORE, TO THE EXTENT PERMITTED BY APPLICABLE LAW, RENESAS ELECTRONICS DISCLAIMS ANY AND ALL WARRANTIES, EXPRESS OR IMPLIED, WITH RESPECT TO THIS DOCUMENT AND ANY RELATED OR ACCOMPANYING SOFTWARE OR HARDWARE, INCLUDING BUT NOT LIMITED TO THE IMPLIED WARRANTIES OF MERCHANTABILITY, OR FITNESS FOR A PARTICULAR PURPOSE.
8. When using Renesas Electronics products, refer to the latest product information (data sheets, user's manuals, application notes, "General Notes for Handling and Using Semiconductor Devices" in the reliability handbook, etc.), and ensure that usage conditions are within the ranges specified by Renesas Electronics with respect to maximum ratings, operating power supply voltage range, heat dissipation characteristics, installation, etc. Renesas Electronics disclaims any and all liability for any malfunctions, failure or accident arising out of the use of Renesas Electronics products outside of such specified ranges.
9. Although Renesas Electronics endeavors to improve the quality and reliability of Renesas Electronics products, semiconductor products have specific characteristics, such as the occurrence of failure at a certain rate and malfunctions under certain use conditions. Unless designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not subject to radiation resistance design. You are responsible for implementing safety measures to guard against the possibility of bodily injury, injury or damage caused by fire, and/or danger to the public in the event of a failure or malfunction of Renesas Electronics products, such as safety design for hardware and software, including but not limited to redundancy, fire control and malfunction prevention, appropriate treatment for aging degradation or any other appropriate measures. Because the evaluation of microcomputer software alone is very difficult and impractical, you are responsible for evaluating the safety of the final products or systems manufactured by you.
10. Please contact a Renesas Electronics sales office for details as to environmental matters such as the environmental compatibility of each Renesas Electronics product. You are responsible for carefully and sufficiently investigating applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive, and using Renesas Electronics products in compliance with all these applicable laws and regulations. Renesas Electronics disclaims any and all liability for damages or losses occurring as a result of your noncompliance with applicable laws and regulations.
11. Renesas Electronics products and technologies shall not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable domestic or foreign laws or regulations. You shall comply with any applicable export control laws and regulations promulgated and administered by the governments of any countries asserting jurisdiction over the parties or transactions.
12. It is the responsibility of the buyer or distributor of Renesas Electronics products, or any other party who distributes, disposes of, or otherwise sells or transfers the product to a third party, to notify such third party in advance of the contents and conditions set forth in this document.
13. This document shall not be reprinted, reproduced or duplicated in any form, in whole or in part, without prior written consent of Renesas Electronics.
14. Please contact a Renesas Electronics sales office if you have any questions regarding the information contained in this document or Renesas Electronics products.

(Note1) "Renesas Electronics" as used in this document means Renesas Electronics Corporation and also includes its directly or indirectly controlled subsidiaries.

(Note2) "Renesas Electronics product(s)" means any product developed or manufactured by or for Renesas Electronics.

(Rev.5.0-1 October 2020)

Corporate Headquarters

TOYOSU FORESIA, 3-2-24 Toyosu,
Koto-ku, Tokyo 135-0061, Japan
www.renesas.com

Trademarks

Renesas and the Renesas logo are trademarks of Renesas Electronics Corporation. All trademarks and registered trademarks are the property of their respective owners.

Contact information

For further information on a product, technology, the most up-to-date version of a document, or your nearest sales office, please visit:
www.renesas.com/contact/.