

Transitioning from RC210xxA (VersaClock) to RC2121xA (AutoClock)

This document describes how to design a PCB to support the transition from RC210xxA (RC21008A, RC21012A) VC7 devices to RC2121xA (RC21211A, RC21212A, RC21213A, RC21214A) AutoClock devices.

Contents

1. Introduction.....	1
2. Device Pinouts.....	2
2.1 48-Pin Devices	2
2.2 40-Pin Devices	3
3. I ² C.....	3
4. Backup Crystal	4
5. GPIO.....	4
6. 3.3V Tolerant.....	4
7. INT and FAULT.....	5
8. 1.2V LVCMOS.....	5
9. LP-HCSL Termination.....	6
10. Revision History	6

1. Introduction

The RC21012A is a 48-pin VFQFPN VersaClock[®] 7 (VC7) clock generator developed primarily for data center applications. The device does not have FuSa features. The RC21211A and RC21212A are 48-pin VFQFPN AutoClock[™] devices with added FuSa features. The 40-pin variants of each device (RC21008A [VC7], RC21213A, RC21214A [AutoClock]) are also referenced in this document.

2. Device Pinouts

2.1 48-Pin Devices

The RC210xxA VC7 and RC2121xA AutoClock are 48-pin VFQFPN devices with many pins in common. Figure 1 shows a mark-up of the device pin commonalities and differences between RC210xxA and RC2121xA.

Legend

- Black text: Common pins for both RC210xxA and RC2121xA devices
- Black with green text: Renamed pin for RC2121xA devices
- Red text with strikethrough: Previous pin name for RC210xxA devices
- Green text: New pin name for RC2121xA devices
- Red text: Renamed pin for RC2121xA devices
- Red with green text: Renamed pin for RC2121xA devices

 


Figure 1. Pinout Differences between 48-VFQFPN RC210xxA and RC2121xA Devices

2.2 40-Pin Devices

The RC21008A and RC21213A/4A are 40-pin VFQFPN devices with many pins in common. Figure 2 shows a mark-up of the device pin commonalities and differences between RC21008A and RC21213A/4A.

Legend

- Black text: Common pins for both RC21008A and RC21213A/4A devices
- Black with green text: Renamed pin for RC21213A/4A devices
- Red text with strikethrough: Previous pin name for RC21008A devices
- Green text: New pin name for RC21213A/4A devices
- Red text: Renamed pin for RC2121xA devices
- Red with green text: Renamed pin for RC21213A/4A devices

 


Figure 2. Pinout Differences between 40-VFQFPN RC21008A and RC21213A/4A Devices

3. I²C

I²C is associated with the SDA and SCL pins. The RC210xxA devices needed be configured to use I²C (not SPI). The RC2121xA devices implement I²C only on the SDA and SCL pins.

4. Backup Crystal

The XOUT1_REFIN1B and XIN1_REFIN1 pins of the following devices make use of a backup crystal.

- RC21012A/08A (VC7) must be configured as GPI with no function assigned; PCB may populate the crystal.
- RC21212A/4A (AutoClock) must be used as backup crystal pins.
- RC21211A/3A (AutoClock) may be used as GPI pins.

5. GPIO

GPIO[4:0] are common to both VC7 and AutoClock devices and must be used as OE (output enable) or SEL (select) as needed. OE can be configured in both devices to enable different outputs as needed. When multiple images are used, the SEL function is used to select which OTP image to load. The RC2121xA devices support up to four OTP images, therefore, no more than four images may be used. In addition, RC210xxA devices must use GPIO[2:0] for SEL.

GPIO[6:5] are new for RC2121xA devices and make use of new functions INT and FAULT.

- RC210xxA (VC7) devices must be configured as GPI with no function assigned.
- RC2121xA (AutoClock) devices must use the GPIO as INT and FAULT pins.

6. 3.3V Tolerant

3.3V tolerant is defined when powering the V_{DD} pin at 1.8V and the GPIO pins being 3.3V tolerant, in other words, an input of 3.3V will not damage the input pad. When powering V_{DD} at 3.3V, digital pins are always 3.3V tolerant.

- VC7 and AutoClock devices support 3.3V tolerant on I²C (in other words, SDA and SCL pins)
- VC7 and AutoClock devices are not 3.3V tolerant on GPI pins
- RC210xxA VC7 devices GPIO pins are *not* 3.3V tolerant
- RC2121xA AutoClock devices GPIO[6:1] pins *are* 3.3 V tolerant
- RC2121xA AutoClock devices GPIO[0] pin is *not* 3.3 V tolerant.

Note: INT and FAULT GPIO[6:5] pins [9:8] are open drain and require an external pull-up.

7. INT and FAULT

Figure 3 shows the recommend schematic for INT and FAULT with input levels to SoC and PMIC being 3.3V. The INT and FAULT pins are open drain and require pull-ups.

- RC210xxA (VC7) does not support INT or FAULT and is *not* 3.3V tolerant
 - R1 = not populated
 - R2 = 10kΩ pull-up
- RC2121xA (AutoClock) supports INT and FAULT and is 3.3V tolerant
 - R1 = 0 ohms
 - R2 = 10kΩ pull-up

 


Figure 3. Interrupt and Fault Schematic

8. 1.2V LVCMOS

Some devices, (for example, UFS) require a 1.2V single-ended clock input. Figure 4 shows VDDO6 is supplied with 1.8V. R2 is either populated, or not to drop voltage at destination, and assumes a 50Ω impedance.

- RC210xxA (VC7) supports 1.8V single-ended
 - R1 = 33Ω, source-series termination
 - R2 = 100Ω, destination termination to reduce voltage from 1.8V to 1.2V
- RC2121xA (AutoClock) supports 1.8V single-ended
 - R1 = 33Ω, source-series termination
 - R2 = 100Ω, destination termination to reduce voltage from 1.8V to 1.2V

 


Figure 4. 1.2V LVCMOS Schematic

9. LP-HCSL Termination

LP-HCSL is series-terminated with 50Ω to match the transmission line (see Figure 5). Other output types use the same termination.

- RC210xxA (VC7) has internal termination of 50Ω
 - $R1 = 0$ ohms
- RC2121xA (AutoClock) requires external termination when using output clock monitoring
 - $R1 = 33\Omega$ combined with the internal source impedance of 17Ω ; total is 50Ω

 


Figure 5. LP-HCSL Termination

10. Revision History

Revision	Date	Description
1.01	Aug 16, 2024	Updated bulleted text for RC2121xA (AutoClock) in section 8.
1.00	Apr 22, 2024	Initial release.

IMPORTANT NOTICE AND DISCLAIMER

RENESAS ELECTRONICS CORPORATION AND ITS SUBSIDIARIES (“RENESAS”) PROVIDES TECHNICAL SPECIFICATIONS AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES “AS IS” AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS OR IMPLIED, INCLUDING, WITHOUT LIMITATION, ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, OR NON-INFRINGEMENT OF THIRD-PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for developers who are designing with Renesas products. You are solely responsible for (1) selecting the appropriate products for your application, (2) designing, validating, and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. Renesas grants you permission to use these resources only to develop an application that uses Renesas products. Other reproduction or use of these resources is strictly prohibited. No license is granted to any other Renesas intellectual property or to any third-party intellectual property. Renesas disclaims responsibility for, and you will fully indemnify Renesas and its representatives against, any claims, damages, costs, losses, or liabilities arising from your use of these resources. Renesas' products are provided only subject to Renesas' Terms and Conditions of Sale or other applicable terms agreed to in writing. No use of any Renesas resources expands or otherwise alters any applicable warranties or warranty disclaimers for these products.

(Disclaimer Rev.1.01)

Corporate Headquarters

TOYOSU FORESIA, 3-2-24 Toyosu,
Koto-ku, Tokyo 135-0061, Japan
www.renesas.com

Trademarks

Renesas and the Renesas logo are trademarks of Renesas Electronics Corporation. All trademarks and registered trademarks are the property of their respective owners.

Contact Information

For further information on a product, technology, the most up-to-date version of a document, or your nearest sales office, please visit www.renesas.com/contact-us/.