

Pipeline vs. Sigma Delta ADC for Communications Applications

Noel O’Riordan, Senior Principal Analog Engineer, Industrial ASIC BU

Introduction

The Analog-to-Digital Converter (ADC) is a key component in digital communications receive channels, and the correct choice of ADC is critical for optimizing system design. In this article, we discuss what design factors drive the selection of the ADC, how to specify the ADC and when to choose between a Pipeline ADC and a Sigma-Delta ($\Sigma\Delta$) ADC.

Contents

Introduction	1
ADC1	
ADC Basics.....	1
Pipeline ADC.....	2
Receive Path Design	3
Specifying the ADC	3
Wideband Wireline.....	3
Broadband Wireless	4
Narrowband Wireless	4
Conclusion	4
Appendix	7
Revision History	8

ADC

Two of the most popular ADC architectures today are the Pipeline ADC and the Sigma-Delta ADC. Traditionally each has had its own distinct application areas, and interestingly, nowadays, there are some areas where both can be applied. We will look at this and determine how to make the appropriate ADC choice.

ADC Basics

To correctly convert a continuous analog signal to its discrete digital representation, the ADC sampling frequency (or sampling rate in MS/s) must be twice the bandwidth of the signal. In practice the input signal’s bandwidth must be limited by an analog ‘Anti-Aliasing’ filter, and the minimum ADC sampling frequency is referred to as the ‘Nyquist frequency’. As we will see, the ADC is often operated at a higher sampling rate to relax the filtering requirements, and the Over-Sampling Ratio (OSR) is the number of times the actual sampling rate is greater than the minimum Nyquist frequency. Converting a continuous analog signal into a discrete digital code, involves unavoidable errors due to quantisation noise, device noise and circuit non-idealities. The number of bits for the ADC is dependent on the Signal-to-Noise-and-Distortion Ratio (SNDR) required in the digital modem decoder. Accurate determination of the SNDR specification is vital for selecting the best ADC: if it is over-dimensioned, the

power and area of the ADC will increase rapidly. Another related key ADC specification is the Effective Number of Bits (ENOB), being the achievable dynamic resolution of the ADC.

Pipeline ADC

A Pipeline ADC consists of a cascade of stages, each of which contains a low-resolution ADC, DAC and amplifier, that successively convert the analog input into its digital representation, while processing the data in a pipe-lined manner. Pipeline ADCs are commonly used for power-efficient high-speed conversion of wide bandwidth input signals (e.g. 10 to 100 MHz). The ADC sampling frequency is usually the Nyquist frequency or lower using small OSRs (e.g. 2 or 4) and the ADC output code resolution is typically between 8 and 14-bit.

The pipeline ADC is an open-loop architecture, having a small inherent latency (e.g. 4 to 6 clock cycles), and a direct relationship between the input signal and the output code. Pipeline ADCs are typically implemented in CMOS processes using Switched Capacitor (SC) discrete-time circuitry. A Pipeline ADC needs a non-trivial analog Anti-Aliasing filter, which consumes additional power and area.

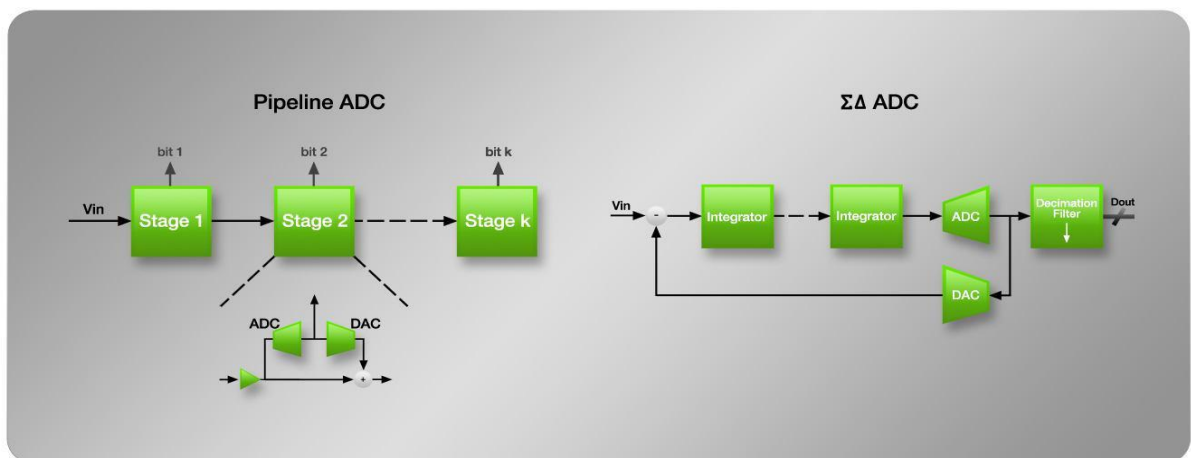


Figure 1: Pipeline and $\Sigma\Delta$ ADC Architectures

ADCs are significantly different from pipeline ADCs and some of the conventional specifications should not be applied directly. They are capable of achieving high ENOB/SNDR (e.g. 10 to 12 ENOB and above), for low to medium input signal bandwidths (e.g. 100kHz to 10MHz).

The architecture employs feedback from the digital to the analog domain and relies on a high OSR (e.g. 10 to 128). The high oversampling ratio allows very simple analog anti-aliasing filters to be used, saving system power and area, but do require some extra digital filtering. As a result of the feedback, the ADC can become unstable for large input signals, and lose performance – so some sort of overload diagnostics are necessary. In addition, there is no direct relationship between the input signal and the digital output code, so dynamic linearity specifications like Spurious Free Dynamic Range (SFDR) are often used instead of Differential and Integral Non-Linearity (DNL/INL).

ADCs can be implemented as Discrete-Time (DT) or Continuous-Time (CT) circuits. Discrete-Time Switched-Capacitor ADCs are easily programmable for different bandwidths, do not require calibration and are relatively insensitive to clock jitter (which can degrade performance). We will focus on DT SC ADCs in this discussion.

Receive Path Design

A typical receive path used in digital communication systems is shown below.

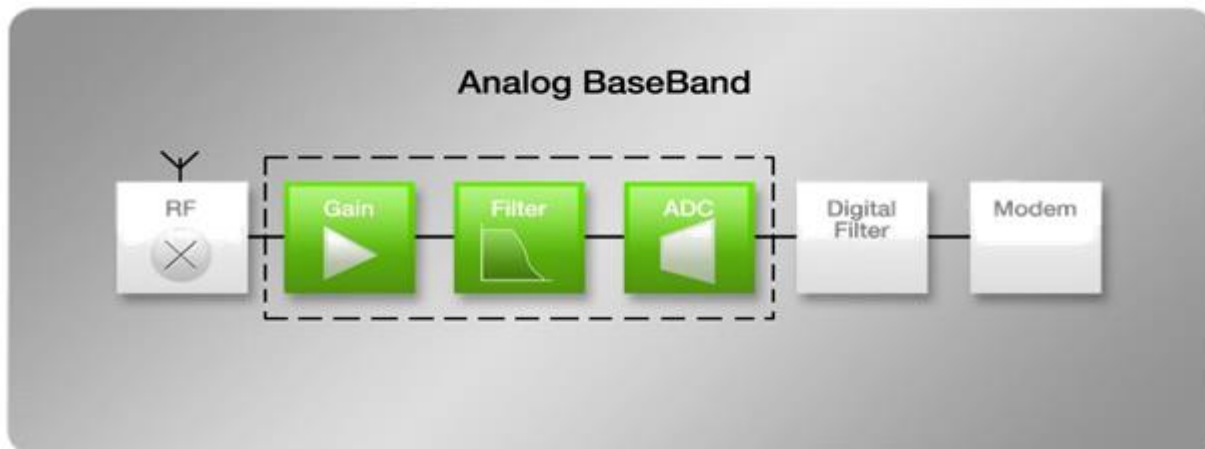


Figure 2: Typical Digital Communications receive path

The Analog Baseband (ABB) is of interest here. Gain is required to amplify the signal. Filtering is required to provide anti-aliasing, by band-limiting the signal presented to the ADC, in order to reduce noise and attenuate interference signals (especially important in wireless applications). In designing such a system, the goal is to trade-off gain, noise linearity, under the constraints of minimising power and die area.

The gain and filtering can be distributed at different points in the receive path. Note that digital communication paths are conveniently implemented by splitting the signal into two components, commonly termed I and Q. For baseband applications, such as wireline communications this can be handled in the digital modem and so only one receive path (and ADC) is needed. For wireless applications, such as WLAN/WiMAX/LTE, the RF down-conversion results in the need for two receive paths and two ADCs, often termed IQ ADC. In the digital domain, some form of decimation filter is typically used, to change the sampling rate down to the Nyquist frequency, irrespective of whether a or a Pipeline ADC is chosen.

Specifying the ADC

Based on the applications standard, the ENOB/SNDR required for the ADC can be calculated. Filtering plays a large role in determining the ADC ENOB. For example, in wireless applications, often one half of the ADC ENOB figure is needed to handle interference signals that may be present. We will consider three applications:

1. Wireband wireline
2. Wireless broadband
3. High-resolution narrow bandwidth wireless

Wideband Wireline

Examples of such applications are Powerline Communications and Cable Modem. The bandwidth is of the order of 40MHz to 100MHz and ENOB required varies from 9.0 to above 10 ENOB. The Pipeline ADC is ideally suited for these applications.

For 9 ENOB and slightly above, a 10-bit Pipeline ADC operating from 8 to 80MS/s can be employed, featuring an area of 0.3mm² while dissipating less than 20mW [1]. For 10 ENOB and above, a 12-bit Pipeline ADC operating at 64MS/s is recommended, typically featuring 0.6mm² and 60mW [2].

Special consideration should also be given to the fact that the input signal is a composite multi-tone OFDM signal and not a simple sine-wave, as has traditionally been used to specify ADCs. The multi-tone nature of OFDM

signals means this signal is in fact composed by a multitude of low-amplitude sinewaves and this has a major impact for example in relaxing the required sampling clock jitter.

Needlessly specifying too high an ENOB for the ADC will result in extra complexity and cost. High ENOBs with sampling rates greater than 100MS/s (e.g. 256MS/s) can be supported with an Interleaved Pipeline approach [3].

Broadband Wireless

Here we will examine two different input signal bandwidths: 4MHz (mobile TV) and 10MHz (LTE). An IQ ADC is used for the two baseband paths after Zero-IF RF down-conversion.

Typical solutions for mobile TV (4MHz) are a 9 ENOB Pipeline ADC operating at OSR of 4 (e.g. 32MS/s sampling rate for the 4MHz bandwidth) or a 10 ENOB ADC with an OSR of 15 (e.g. 120MS/s sampling rate for the 4MHz bandwidth). Good examples of Pipeline and ADCs [4, 5] show similar areas (0.65mm²) but the pipeline solution features less than half the power (15mW versus 37mW) mainly due to the lower ENOB of 9 versus 10 for the ADC. So, the architecture choice here is based mainly on system level architecture. The ADC allows the order of the analog anti-aliasing filter to be reduced by 3, saving up to 1.0mm² and 10mW. A digital decimating filter is needed for both types of ADCs, with the needing an extra digital filtering stage that consumes 1mW, but negligible area. Both ADCs need a buffer before them to drive the sampling capacitor, and in the case of a ADC additional anti-aliasing filtering can be easily incorporated into this buffer at little cost. In this instance, the ADC can provide a lower area receive path solution.

For a 10MHz input bandwidth, a typical implementation uses a 9 ENOB IQ Pipeline ADC sampling at 80MS/s (OSR=4) and consuming 40mW [4], or a ADC with similar ENOB performance sampling at 180MS/s (OSR=9) and consuming 45mW [6]. In this case, the choice depends more on the customer preference and the possible need for compatibility with higher bandwidths in the future, which might tend to favour a Pipeline ADC.

For higher ENOBs at 10MHz input bandwidth and above, for example 10.5ENOB as often required in LTE, a 12-bit Pipeline Dual Input IQ ADC sampling each channel at 32MS/s seems to be a good solution, featuring 58mW and 0.65mm² for complete IQ solution [7].

Narrowband Wireless

High resolutions of 11-12 ENOB are required in bandwidths of a few hundred kHz for standards like GSM. In order to achieve such high-performance levels, a pipeline ADC will require calibration, whereas a IQ ADC can provide this resolution while consuming only 7.5mW [8].

For multi-standard receivers, such as Software Defined Radio, an ADC is the favoured architecture, due to its ease of programmability over a wide range of ENOB/SNDR requirements.

Conclusion

Choosing the correct ADC is a crucial step in designing the optimum receive path, and attention must be paid to accurately specify the ADC by taking the full system into consideration. The information provide in this article should prove useful in making this selection.

At Renesas, formerly Dialog, we have a comprehensive offering of high performance, low power, silicon proven ADC's for pipeline and architectures covering input bandwidths from 100kHz to 100MHz, in advanced deep sub-micron technologies and in multiple foundry processes.

 


Figure 3: Performance range of Pipeline and ΣΔ ADCs



Table 1: Comparison points for choice of Pipeline or SD ADCs

Design Issue	Pipeline ADC	$\Sigma\Delta$ ADC
Input Bandwidth	Up to 100 MHz	Up to 10MHz
Effective Resolution (ENOB)	9-10.5 ENOB (without calibration) 11 ENOB (with calibration)	10-12 ENOB (without calibration)
System Filtering	Analog Anti - Aliasing Digital FIR	Much reduced analog filtering Digital FIR + additional CIC filter
System Gain	Analog Programmable Gain	Reduced Analog Programmable Gain possible
Latency	5 -6 clock cycles	Lower than pipeline
Maximum Input Signal	No stability issues	Large inputs can degrade ENOB by overloading ADC, which should have a diagnostic output
Application Areas	802.11x DVB - TH, DMB WiMax LTE Docsis HDTV HomePlug Imaging	DVB-H/, DMB WiMax SDR DAB UMTS CDMA GSM LTE

Appendix

Mixed-Signal IP Parts Quoted in this Article:

[1] S3AD88M10BC90

[2] S3AD64M12BT65D

[3] S3AD256M12BT65

[4] S3ADIQ88M10BC90

[5] S3AD120M11BC90

[6] S3ADIQ180M10BSM90LP

[7] S3AD64MD12BT65D

[8] S3ADIQ160MSDC13

Revision History

Revision	Date	Description
1.0	Oct 01, 2015	Initial release
1.1	Dec 22, 2021	Re-brand