

IGBT

Renesas IGBT SPICE model

About this document

This document will describe the IGBT SPICE model provided by Renesas

Target Device

IGBT

Contents

1. Introduction.....	2
2. IGBT SPICE MODEL.....	2
2.1 Supported Simulators.....	2
2.2 Grades of SPICE model.....	2
2.3 Encryption.....	2
2.4 Topology.....	3
3. Accuracy Comparison.....	4
3.1 DC & Temperature	4
3.2 Capacitance.....	4
3.3 Switching	5
Revision History.....	7

1. Introduction

In recent years, heat and noise caused by power devices have become an issue in the development of applications that incorporate power devices, and simulation is becoming more important to shorten development time. SPICE, a circuit simulator, can perform various calculations such as power loss calculation of power devices, prediction of gate drive performance, circuit avalanche energy, switching time, and transient junction temperature rise.

Since there is no standard SPICE model for power devices, power device manufacturers develop their own models and provide them to users. This paper describes the features of Renesas SPICE model for IGBTs.

2. IGBT SPICE MODEL

2.1 Supported Simulators

There are many types of commercial circuit simulators. Renesas provides SPICE models for the following simulators (Table 2-1), which are mainstream in the field of power electronics.

Table 2-1 Supported Simulators

Name	Vendor
PSPICE	Cadence
LTspice	Analog Devices
Simetrix	SIMetrix Technologies Ltd

2.2 Grades of SPICE model

As mentioned in the Introduction, SPICE models for power devices must be developed independently by the manufacturer. To obtain high simulation accuracy, SPICE models need to be complex, but this in turn reduces simulation speed and worsens calculation convergence. Therefore, two types of SPICE models are offered: a simple SPICE model (G1 model) that emphasizes calculation speed and a high-precision SPICE model (G2 model) that emphasizes accuracy (Table 2-2)

Table 2-2 Grades of SPICE model

Grade	Encryption	Features
G1	Non-encryption	emphasizes calculation speed and convergence
G2	Encryption	emphasizes calculation accuracy

2.3 Encryption

SPICE models contain confidential information such as modeling techniques to accurately represent device characteristics and device structures. Therefore, G2 models, which are high-precision SPICE models, are encrypted and published. Encrypted models can only be used on the target simulator and cannot be edited at all, which is not convenient for users. Therefore, for user convenience, the G1 model, which is a simple SPICE model, is published without encryption.


2.4 Topology

The G1 model is a model consisting of a minimum number of elements to represent the basic operation of IGBTs in order to prioritize calculation speed.

The G2 model consists of a large number of elements to analyze switching characteristics with high accuracy.

Among the parasitic components of the package, resistance and capacitance components are included in the SPICE model, but inductance components are not.

G1 SPICE Model

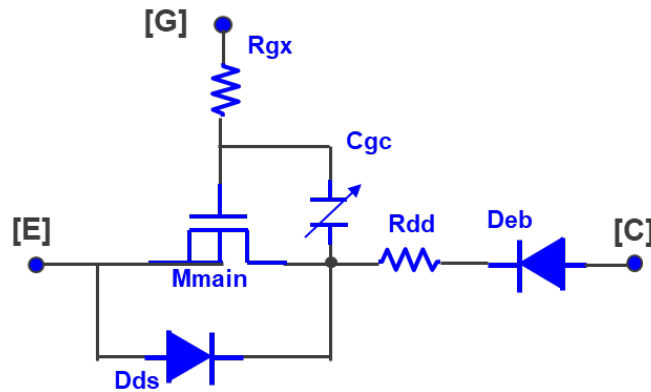

G2 SPICE Model

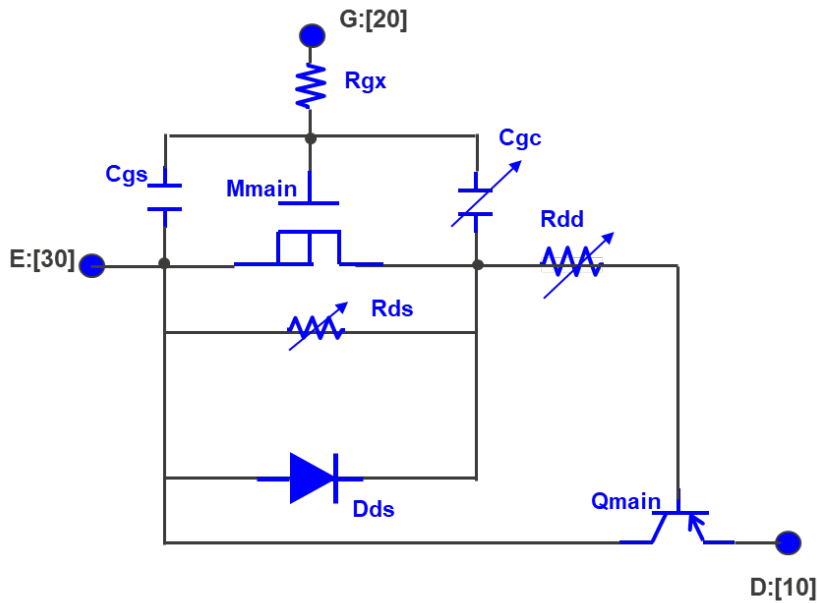


Figure 2-1 Topology of IGBT SPICE models

3. Accuracy Comparison

3.1 DC & Temperature

The accuracy comparison of the G1 and G2 SPICE models using Renesas 8th generation IGBTs (1800V class) as the subject of actual measurements are shown in Figure 3-1. The G1 model shows the overall trend, but as VGS increases, the transition from linear to saturation deviates from the actual measurement, and this trend increases as temperature increases. On the other hand, the G2 model agrees well with the actual measurement under all conditions because BSIM3 is used for the MOS model and the bias dependence of the drift resistance is modeled

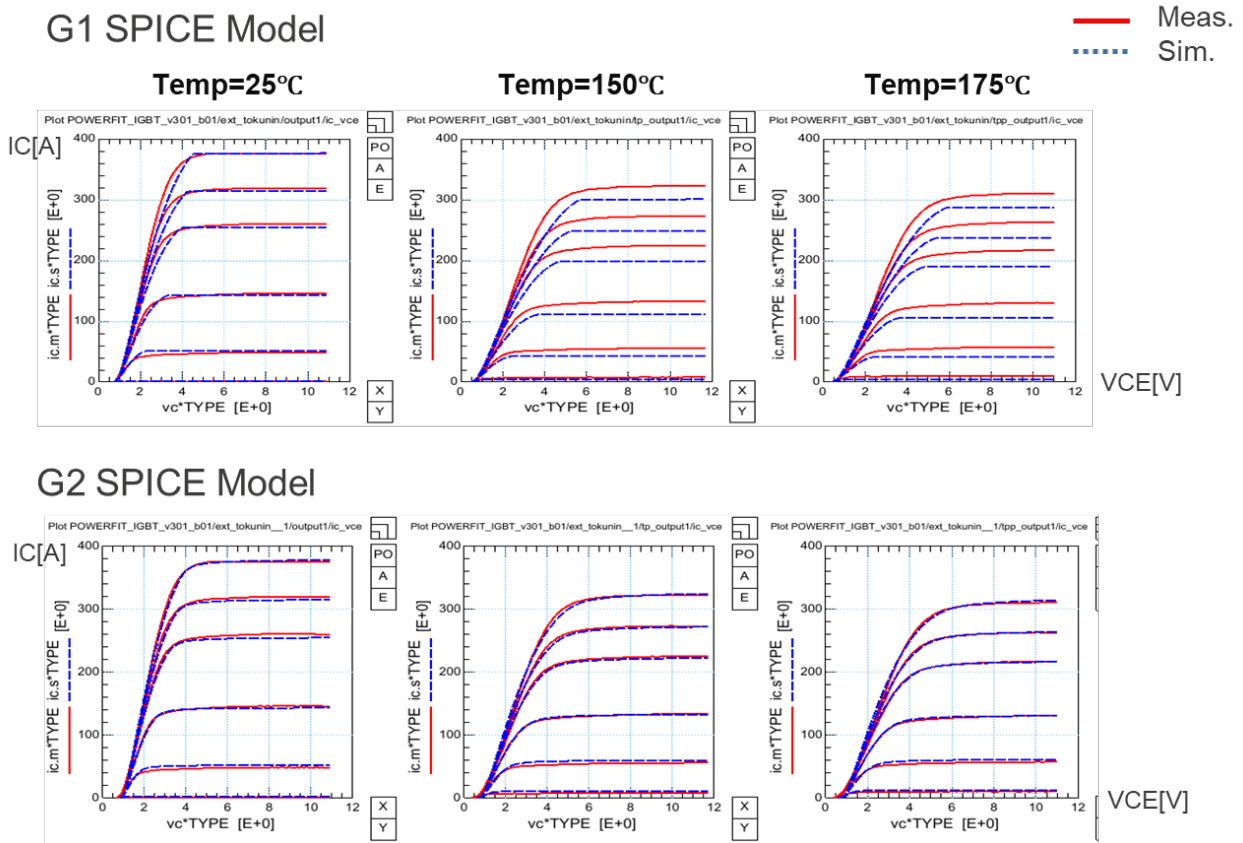


Figure 3-1 Comparison of modeling accuracy of DC characteristics (G1 vs. G2 model)

3.2 Capacitance

It is known that the general PN junction capacitance decreases with \sqrt{V} with respect to voltage. Cres and Coes of classical IGBTs show bias dependence according to this theory. However, as IGBTs continue to change their device structure and achieve improved device performance, the device structure becomes more complex with each successive generation. As a result, the capacitance shows a very complicated bias dependence. The solid lines in the figure show the VDS dependence of Cres, Cies, and Coes. The G1 model shows a decrease in capacitance with increasing VDS, but not a change in trend. The G2 model, on the other hand, shows a change in the bias-dependent trend of capacitance with a boundary of about 0.5 V.

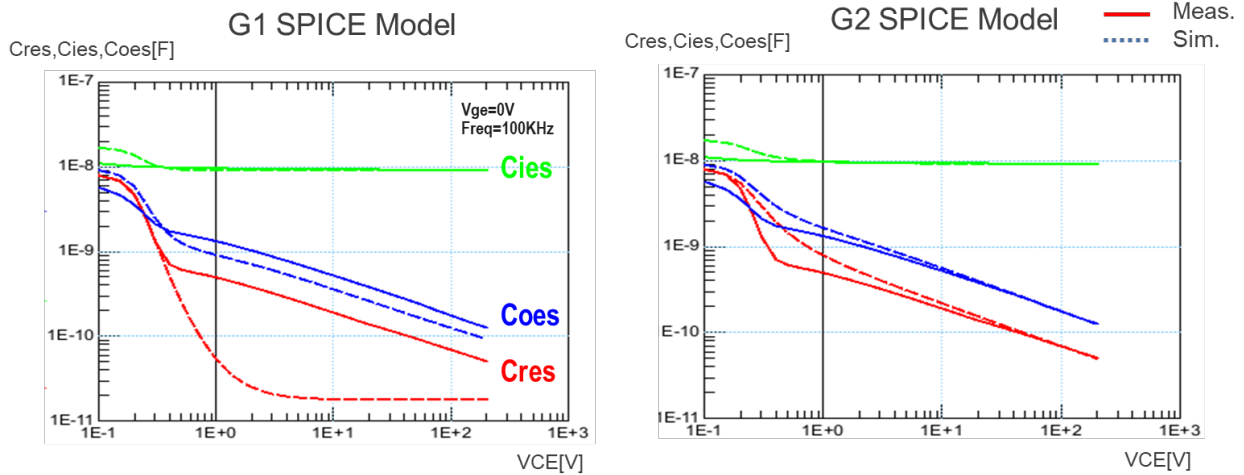


Figure 3-2 Comparison of modeling accuracy of CV characteristics (G1 vs. G2 model)

3.3 Switching

IGBTs are mainly used in inverter circuits for motor drives, so accuracy under inductive load is important. In addition, it is necessary to select the optimum external gate resistance value for each application, and it is important to ensure high simulation accuracy even when the gate resistance value fluctuates.


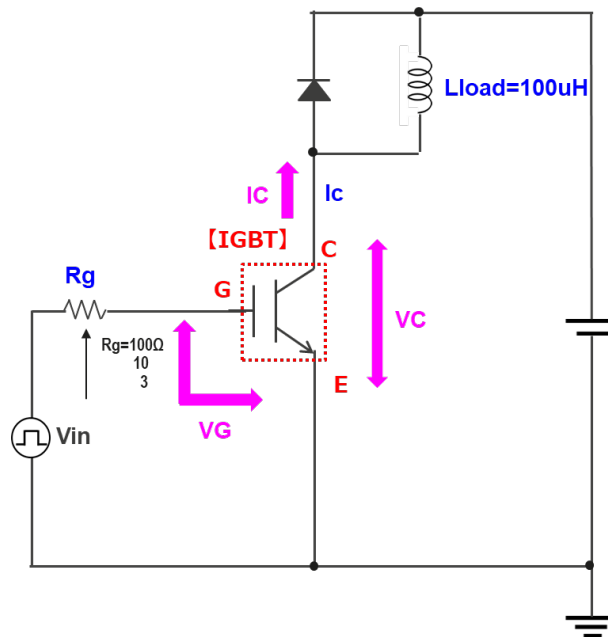


Figure 3-3 Switching Test bench

Figure 3-4 and Figure 3-5 show the switching characteristics (Turn-Off and Turn-On) when the external RG is changed (RG=3, 10, 100Ω), red is the actual measurement and blue is the simulation. The G1 model shows a tendency for switching to slow down as RG increases, but the slopes do not match at all, resulting in a large error in loss. On the other hand, the G2 model shows the bias dependence of capacitance and the introduction of a special model to match switching, and thus shows with high accuracy the tendency for switching characteristics to vary with gate resistance, including losses.

G1 SPICE Model

— Meas.
 - - - Sim.

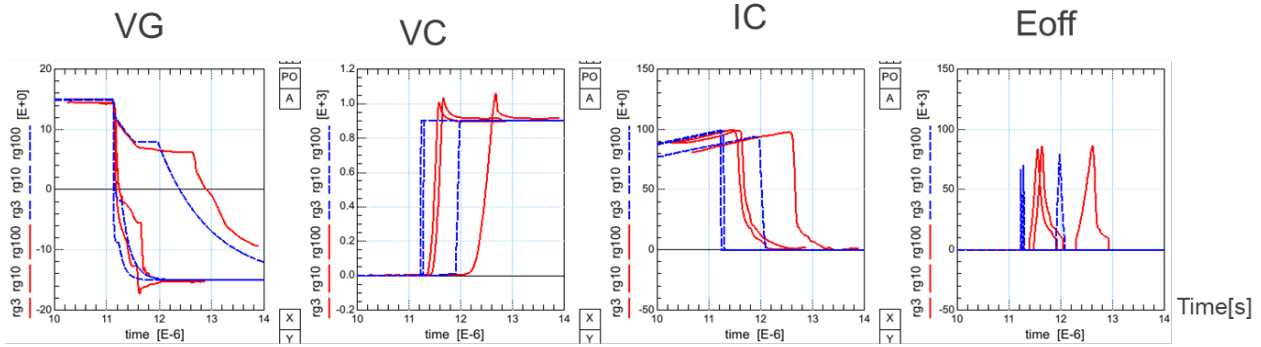

G2 SPICE Model


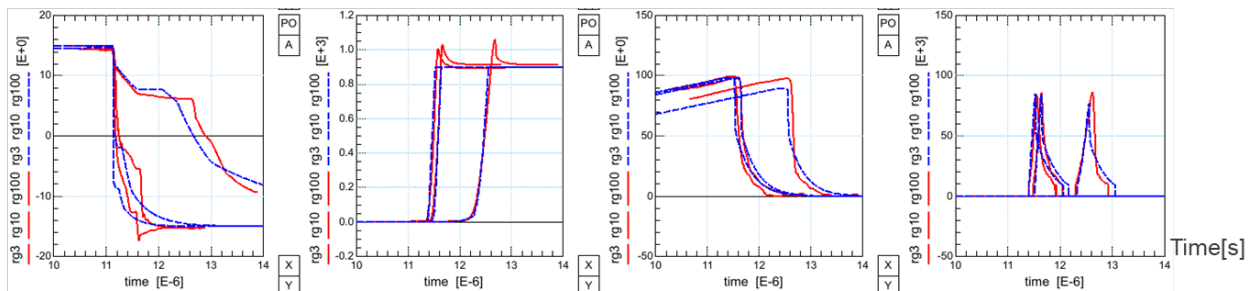


Figure 3-4 Comparison of modeling accuracy of Turn-off characteristics (G1 vs. G2 model)

G1 SPICE Model

— Meas.
 - - - Sim.

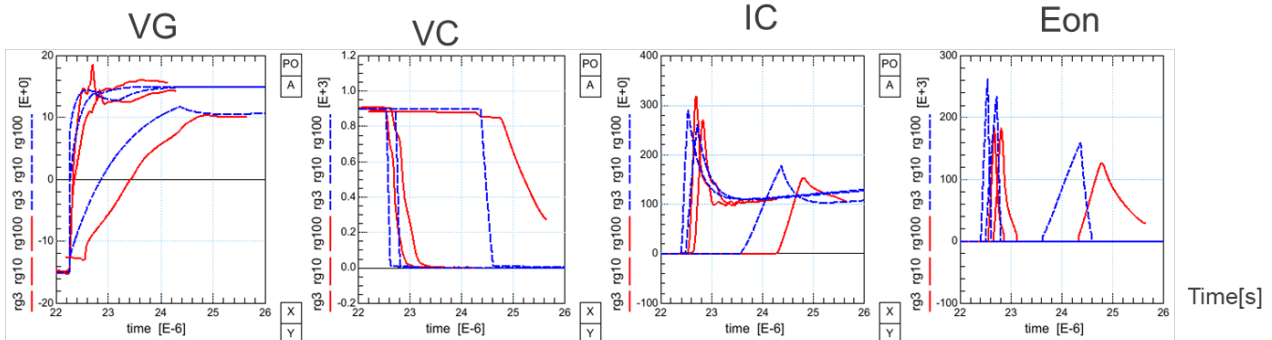

G2 SPICE Model

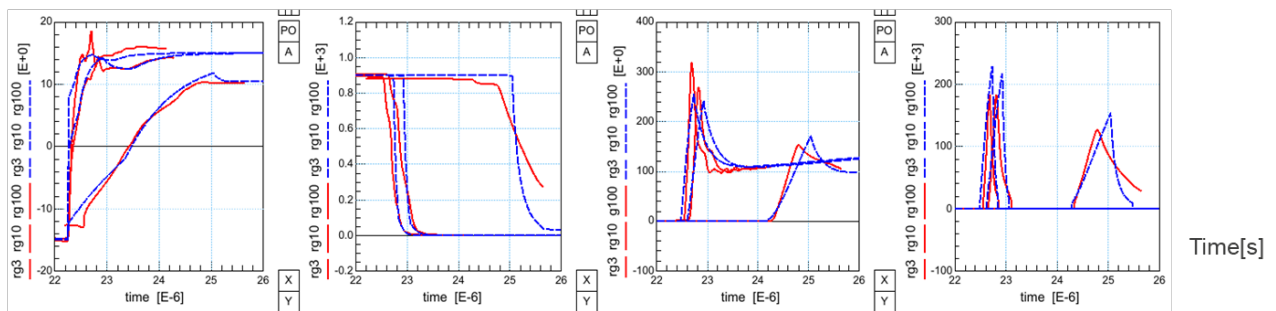


Figure 3-5 Comparison of modeling accuracy of Turn-on characteristics (G1 vs. G2 model)

Revision History

Rev.	Date	Description	
		Page	Summary
1.00	Sep.11.2024	-	First edition

Notice

1. Descriptions of circuits, software and other related information in this document are provided only to illustrate the operation of semiconductor products and application examples. You are fully responsible for the incorporation or any other use of the circuits, software, and information in the design of your product or system. Renesas Electronics disclaims any and all liability for any losses and damages incurred by you or third parties arising from the use of these circuits, software, or information.
2. Renesas Electronics hereby expressly disclaims any warranties against and liability for infringement or any other claims involving patents, copyrights, or other intellectual property rights of third parties, by or arising from the use of Renesas Electronics products or technical information described in this document, including but not limited to, the product data, drawings, charts, programs, algorithms, and application examples.
3. No license, express, implied or otherwise, is granted hereby under any patents, copyrights or other intellectual property rights of Renesas Electronics or others.
4. You shall be responsible for determining what licenses are required from any third parties, and obtaining such licenses for the lawful import, export, manufacture, sales, utilization, distribution or other disposal of any products incorporating Renesas Electronics products, if required.
5. You shall not alter, modify, copy, or reverse engineer any Renesas Electronics product, whether in whole or in part. Renesas Electronics disclaims any and all liability for any losses or damages incurred by you or third parties arising from such alteration, modification, copying or reverse engineering.
6. Renesas Electronics products are classified according to the following two quality grades: "Standard" and "High Quality". The intended applications for each Renesas Electronics product depends on the product's quality grade, as indicated below.
 - "Standard": Computers; office equipment; communications equipment; test and measurement equipment; audio and visual equipment; home electronic appliances; machine tools; personal electronic equipment; industrial robots; etc.
 - "High Quality": Transportation equipment (automobiles, trains, ships, etc.); traffic control (traffic lights); large-scale communication equipment; key financial terminal systems; safety control equipment; etc.

Unless expressly designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not intended or authorized for use in products or systems that may pose a direct threat to human life or bodily injury (artificial life support devices or systems; surgical implantations; etc.), or may cause serious property damage (space system; undersea repeaters; nuclear power control systems; aircraft control systems; key plant systems; military equipment; etc.). Renesas Electronics disclaims any and all liability for any damages or losses incurred by you or any third parties arising from the use of any Renesas Electronics product that is inconsistent with any Renesas Electronics data sheet, user's manual or other Renesas Electronics document.
7. No semiconductor product is absolutely secure. Notwithstanding any security measures or features that may be implemented in Renesas Electronics hardware or software products, Renesas Electronics shall have absolutely no liability arising out of any vulnerability or security breach, including but not limited to any unauthorized access to or use of a Renesas Electronics product or a system that uses a Renesas Electronics product. RENESAS ELECTRONICS DOES NOT WARRANT OR GUARANTEE THAT RENESAS ELECTRONICS PRODUCTS, OR ANY SYSTEMS CREATED USING RENESAS ELECTRONICS PRODUCTS WILL BE INVULNERABLE OR FREE FROM CORRUPTION, ATTACK, VIRUSES, INTERFERENCE, HACKING, DATA LOSS OR THEFT, OR OTHER SECURITY INTRUSION ("Vulnerability Issues"). RENESAS ELECTRONICS DISCLAIMS ANY AND ALL RESPONSIBILITY OR LIABILITY ARISING FROM OR RELATED TO ANY VULNERABILITY ISSUES. FURTHERMORE, TO THE EXTENT PERMITTED BY APPLICABLE LAW, RENESAS ELECTRONICS DISCLAIMS ANY AND ALL WARRANTIES, EXPRESS OR IMPLIED, WITH RESPECT TO THIS DOCUMENT AND ANY RELATED OR ACCOMPANYING SOFTWARE OR HARDWARE, INCLUDING BUT NOT LIMITED TO THE IMPLIED WARRANTIES OF MERCHANTABILITY, OR FITNESS FOR A PARTICULAR PURPOSE.
8. When using Renesas Electronics products, refer to the latest product information (data sheets, user's manuals, application notes, "General Notes for Handling and Using Semiconductor Devices" in the reliability handbook, etc.), and ensure that usage conditions are within the ranges specified by Renesas Electronics with respect to maximum ratings, operating power supply voltage range, heat dissipation characteristics, installation, etc. Renesas Electronics disclaims any and all liability for any malfunctions, failure or accident arising out of the use of Renesas Electronics products outside of such specified ranges.
9. Although Renesas Electronics endeavors to improve the quality and reliability of Renesas Electronics products, semiconductor products have specific characteristics, such as the occurrence of failure at a certain rate and malfunctions under certain use conditions. Unless designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not subject to radiation resistance design. You are responsible for implementing safety measures to guard against the possibility of bodily injury, injury or damage caused by fire, and/or danger to the public in the event of a failure or malfunction of Renesas Electronics products, such as safety design for hardware and software, including but not limited to redundancy, fire control and malfunction prevention, appropriate treatment for aging degradation or any other appropriate measures. Because the evaluation of microcomputer software alone is very difficult and impractical, you are responsible for evaluating the safety of the final products or systems manufactured by you.
10. Please contact a Renesas Electronics sales office for details as to environmental matters such as the environmental compatibility of each Renesas Electronics product. You are responsible for carefully and sufficiently investigating applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive, and using Renesas Electronics products in compliance with all these applicable laws and regulations. Renesas Electronics disclaims any and all liability for damages or losses occurring as a result of your noncompliance with applicable laws and regulations.
11. Renesas Electronics products and technologies shall not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable domestic or foreign laws or regulations. You shall comply with any applicable export control laws and regulations promulgated and administered by the governments of any countries asserting jurisdiction over the parties or transactions.
12. It is the responsibility of the buyer or distributor of Renesas Electronics products, or any other party who distributes, disposes of, or otherwise sells or transfers the product to a third party, to notify such third party in advance of the contents and conditions set forth in this document.
13. This document shall not be reprinted, reproduced or duplicated in any form, in whole or in part, without prior written consent of Renesas Electronics.
14. Please contact a Renesas Electronics sales office if you have any questions regarding the information contained in this document or Renesas Electronics products.

(Note1) "Renesas Electronics" as used in this document means Renesas Electronics Corporation and also includes its directly or indirectly controlled subsidiaries.

(Note2) "Renesas Electronics product(s)" means any product developed or manufactured by or for Renesas Electronics.

(Rev.5.0-1 October 2020)

Corporate Headquarters

TOYOSU FORESIA, 3-2-24 Toyosu,
Koto-ku, Tokyo 135-0061, Japan
www.renesas.com

Trademarks

Renesas and the Renesas logo are trademarks of Renesas Electronics Corporation. All trademarks and registered trademarks are the property of their respective owners.

Contact information

For further information on a product, technology, the most up-to-date version of a document, or your nearest sales office, please visit:
www.renesas.com/contact/.