

### Introduction

You can use variable-gain amplifiers (VGAs) in many types of systems, such as radio receivers, in which the input signal voltage depends on an uncontrolled variable, such as distance to the transmitter. In this type of system, you can use a VGA to ensure that the input signal amplitude matches the input voltage range of key components, such as ADCs and DACs, thereby maximizing the converters' dynamic range. The VGA in Figure 1 has high bandwidth, ranging from 115MHz at high gain to 225MHz at low gain, so you can use this circuit in the RF-signal path without degrading the signal. You can update the DAC in this circuit at 100MHz, but the level-shifter op amp limits the speed at which you can update the gain of the VGA to 3MHz. As configured, this VGA implements a calibration function with a 3MHz DAC update rate.

The VGA design comprises a three-transistor, long-tailed pair configuration comprising  $Q_1$ ,  $Q_2$ , and  $Q_3$ . By changing the base voltage of  $Q_3$ , the DAC ( $IC_1$ ) varies the emitter currents of the long-tailed pair. Changing  $Q_3$ 's base voltage controls the gain according to the following equation, where  $K$  is a function of the emitter current and  $V_{B3}$  is the base voltage of  $Q_3$ :

$$G = KV_{IN}|V_{B3}|.$$

The gain control and bias-stability parameters of the circuit depend on transistor matching, so the circuit uses an HFA3102 matched, long-tailed array for  $Q_1$  through  $Q_3$ . The usable range of  $V_{B3}$  is -0.8 to -4.4V, which corresponds to a gain range of 11.8 to -16.9dB, respectively. This gain span is a total of 28.7dB. The gain is proportional to  $R_4$ . Increasing  $R_4$  increases the gain, but the gain span stays constant at approximately 28.7dB. Increasing the gain causes a corresponding decrease in the frequency response.

$R_2$ ,  $R_3$ , and the -5V supply form a bias circuit that sets  $V_{B3}$  to -4.4V when there is no DAC output current (the voltage across  $R_1$  is zero), which occurs at a digital input of all ones. When the digital input is all zeros, the DAC output current is 20mA, which develops -1V across  $R_1$ .  $IC_2$  level-shifts and amplifies this voltage to yield  $V_{B3} = -0.8V$ . The CA5160 works well as the level shifter because its low bias currents do not affect the DC performance, and its bandwidth enables the gain to change at a rate as high as 3MHz.

You should keep the video input signal level at about 25mV to prevent distortion. The signal path has an excellent frequency response because the HFA3102 is the only component in the signal path. A frequency response plot for  $V_{B3} = -3V$  (gain of 10dB) shows that the transfer function is well-behaved with no peaking and that the frequency response is 131MHz at the -3dB point. The DAC transfers the digital input to the internal registers on the rising edge of the clock pulses. This circuit uses the inverting DAC output to yield a positive increasing-transfer function, but you can obtain the inverse-transfer function by using the noninverting input (Table 1).

**TABLE 1. VGA PERFORMANCE SUMMARY**

PARAMETER	MINIMUM	MAXIMUM
Gain (dB)	-16.9	11.8
$V_{B3}$ (V)	-4.4	-0.8
$F_{-3dB}$ (MHz)	225	115
Digital Input/Inverting Output	0000 0000 0000	1111 1111 1111
Digital Input/Noninverting Output	1111 1111 1111	0000 0000 0000

If fast updates are unnecessary, you can use a slower DAC than  $IC_1$ . However, you may also have to redesign the interface circuit ( $IC_2$  and associated components) if the DAC output voltage swing changes.

## Notice

1. Descriptions of circuits, software and other related information in this document are provided only to illustrate the operation of semiconductor products and application examples. You are fully responsible for the incorporation or any other use of the circuits, software, and information in the design of your product or system. Renesas Electronics disclaims any and all liability for any losses and damages incurred by you or third parties arising from the use of these circuits, software, or information.
2. Renesas Electronics hereby expressly disclaims any warranties against and liability for infringement or any other claims involving patents, copyrights, or other intellectual property rights of third parties, by or arising from the use of Renesas Electronics products or technical information described in this document, including but not limited to, the product data, drawings, charts, programs, algorithms, and application examples.
3. No license, express, implied or otherwise, is granted hereby under any patents, copyrights or other intellectual property rights of Renesas Electronics or others.
4. You shall not alter, modify, copy, or reverse engineer any Renesas Electronics product, whether in whole or in part. Renesas Electronics disclaims any and all liability for any losses or damages incurred by you or third parties arising from such alteration, modification, copying or reverse engineering.
5. Renesas Electronics products are classified according to the following two quality grades: "Standard" and "High Quality". The intended applications for each Renesas Electronics product depends on the product's quality grade, as indicated below.  
"Standard": Computers; office equipment; communications equipment; test and measurement equipment; audio and visual equipment; home electronic appliances; machine tools; personal electronic equipment; industrial robots; etc.  
"High Quality": Transportation equipment (automobiles, trains, ships, etc.); traffic control (traffic lights); large-scale communication equipment; key financial terminal systems; safety control equipment; etc.  
Unless expressly designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not intended or authorized for use in products or systems that may pose a direct threat to human life or bodily injury (artificial life support devices or systems; surgical implantations; etc.), or may cause serious property damage (space system; undersea repeaters; nuclear power control systems; aircraft control systems; key plant systems; military equipment; etc.). Renesas Electronics disclaims any and all liability for any damages or losses incurred by you or any third parties arising from the use of any Renesas Electronics product that is inconsistent with any Renesas Electronics data sheet, user's manual or other Renesas Electronics document.
6. When using Renesas Electronics products, refer to the latest product information (data sheets, user's manuals, application notes, "General Notes for Handling and Using Semiconductor Devices" in the reliability handbook, etc.), and ensure that usage conditions are within the ranges specified by Renesas Electronics with respect to maximum ratings, operating power supply voltage range, heat dissipation characteristics, installation, etc. Renesas Electronics disclaims any and all liability for any malfunctions, failure or accident arising out of the use of Renesas Electronics products outside of such specified ranges.
7. Although Renesas Electronics endeavors to improve the quality and reliability of Renesas Electronics products, semiconductor products have specific characteristics, such as the occurrence of failure at a certain rate and malfunctions under certain use conditions. Unless designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not subject to radiation resistance design. You are responsible for implementing safety measures to guard against the possibility of bodily injury, injury or damage caused by fire, and/or danger to the public in the event of a failure or malfunction of Renesas Electronics products, such as safety design for hardware and software, including but not limited to redundancy, fire control and malfunction prevention, appropriate treatment for aging degradation or any other appropriate measures. Because the evaluation of microcomputer software alone is very difficult and impractical, you are responsible for evaluating the safety of the final products or systems manufactured by you.
8. Please contact a Renesas Electronics sales office for details as to environmental matters such as the environmental compatibility of each Renesas Electronics product. You are responsible for carefully and sufficiently investigating applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive, and using Renesas Electronics products in compliance with all these applicable laws and regulations. Renesas Electronics disclaims any and all liability for damages or losses occurring as a result of your noncompliance with applicable laws and regulations.
9. Renesas Electronics products and technologies shall not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable domestic or foreign laws or regulations. You shall comply with any applicable export control laws and regulations promulgated and administered by the governments of any countries asserting jurisdiction over the parties or transactions.
10. It is the responsibility of the buyer or distributor of Renesas Electronics products, or any other party who distributes, disposes of, or otherwise sells or transfers the product to a third party, to notify such third party in advance of the contents and conditions set forth in this document.
11. This document shall not be reprinted, reproduced or duplicated in any form, in whole or in part, without prior written consent of Renesas Electronics.
12. Please contact a Renesas Electronics sales office if you have any questions regarding the information contained in this document or Renesas Electronics products.  
(Note 1) "Renesas Electronics" as used in this document means Renesas Electronics Corporation and also includes its directly or indirectly controlled subsidiaries.  
(Note 2) "Renesas Electronics product(s)" means any product developed or manufactured by or for Renesas Electronics.

(Rev.4.0-1 November 2017)



### SALES OFFICES

Renesas Electronics Corporation

<http://www.renesas.com>

Refer to "<http://www.renesas.com/>" for the latest and detailed information.

**Renesas Electronics America Inc.**  
1001 Murphy Ranch Road, Milpitas, CA 95035, U.S.A.  
Tel: +1-408-432-8888, Fax: +1-408-434-5351

**Renesas Electronics Canada Limited**  
9251 Yonge Street, Suite 8309 Richmond Hill, Ontario Canada L4C 9T3  
Tel: +1-905-237-2004

**Renesas Electronics Europe Limited**  
Dukes Meadow, Millboard Road, Bourne End, Buckinghamshire, SL8 5FH, U.K  
Tel: +44-1628-651-700, Fax: +44-1628-651-804

**Renesas Electronics Europe GmbH**  
Arcadiastrasse 10, 40472 Düsseldorf, Germany  
Tel: +49-211-6503-0, Fax: +49-211-6503-1327

**Renesas Electronics (China) Co., Ltd.**  
Room 1709 Quantum Plaza, No.27 ZhichunLu, Haidian District, Beijing, 100191 P. R. China  
Tel: +86-10-8235-1155, Fax: +86-10-8235-7679

**Renesas Electronics (Shanghai) Co., Ltd.**  
Unit 301, Tower A, Central Towers, 555 Langao Road, Putuo District, Shanghai, 200333 P. R. China  
Tel: +86-21-2226-0888, Fax: +86-21-2226-0999

**Renesas Electronics Hong Kong Limited**  
Unit 1601-1611, 16/F., Tower 2, Grand Century Place, 193 Prince Edward Road West, Mongkok, Kowloon, Hong Kong  
Tel: +852-2265-6688, Fax: +852-2886-9022

**Renesas Electronics Taiwan Co., Ltd.**  
13F, No. 363, Fu Shing North Road, Taipei 10543, Taiwan  
Tel: +886-2-8175-9600, Fax: +886-2-8175-9670

**Renesas Electronics Singapore Pte. Ltd.**  
80 Bendemeer Road, Unit #06-02 Hyflux Innovation Centre, Singapore 339949  
Tel: +65-6213-0200, Fax: +65-6213-0300

**Renesas Electronics Malaysia Sdn.Bhd.**  
Unit 1207, Block B, Menara Amcorp, Amcorp Trade Centre, No. 18, Jln Persiaran Barat, 46050 Petaling Jaya, Selangor Darul Ehsan, Malaysia  
Tel: +60-3-7955-9390, Fax: +60-3-7955-9510

**Renesas Electronics India Pvt. Ltd.**  
No.777C, 100 Feet Road, HAL 2nd Stage, Indiranagar, Bangalore 560 038, India  
Tel: +91-80-67208700, Fax: +91-80-67208777

**Renesas Electronics Korea Co., Ltd.**  
17F, KAMCO Yangjae Tower, 262, Gangnam-daero, Gangnam-gu, Seoul, 06265 Korea  
Tel: +82-2-558-3737, Fax: +82-2-558-5338