

Application Note

DA9313 Frequently Asked Questions

AN-PM-090

Abstract

Using a question-and-answer format, this application note presents solutions to various application topics when designing-in the DA9313 into a system.

DA9313 Frequently Asked Questions**Contents**

Abstract	1
Contents	2
1 Terms and Definitions	3
2 References	3
3 Introduction	4
4 Frequently Asked Questions	4
4.1 External Components.....	4
4.2 Power Voltage Converter	4
4.3 I ² C Compatible Interface	5
4.4 Other	6
Revision History	8

DA9313 Frequently Asked Questions

1 Terms and Definitions

OVP	Over Voltage Protection
PVC	Power Voltage Converter
SoC	System on Chip
OD	Open Drain

2 References

- [1] DA9313 Datasheet, Rev 3.0, Dialog Semiconductor
- [2] ER-PM-003, DA9313 Startup Considerations, Rev 1.0, Dialog Semiconductor

DA9313 Frequently Asked Questions

3 Introduction

The purpose of this applications note is to help customers understand the various aspects of the DA9313 converter when designed into their systems.

4 Frequently Asked Questions

4.1 External Components

1. Could the flying capacitor value or quantity be reduced?

Reducing the flying capacitor value will impact efficiency. Reducing the quantity of capacitors may impact reliability. The flying capacitor must have the appropriate ripple current rating to meet the maximum 20 °C temperature rise requirement.

2. What is the flying capacitors (C_{FLY}) effective capacitance?

C_{FLY} per phase must be rated to $\geq 18 \mu F @ 5 V, I_{RMS} = 8 A$. For a lower output load current, contact ic-support@diasemi.com for technical support.

Note that there are two C_{FLY} in parallel per phase, therefore each capacitor must be rated to $\geq 9 \mu F @ 5 V, I_{RMS} = 4 A$.

3. What is the V_{CORE} capacitor (CO_V_{CORE}) effective capacitance?

The external CO_V_{CORE} effective capacitance should be min 0.5 μF , max 1.3 μF and is typically 1.0 μF .

What are VIN to VOUT and VOUT to GND decoupling capacitors used for? Could I reduce their values?

They are used to decouple the internal FET drivers that are connected to VIN, VOUT and GND.

The VIN to VOUT capacitor value could be reduced to 1 μF because there should be a localized decoupling to VIN (2 * 4.7 μF or 1 * 10 μF as recommended in the datasheet). The VOUT to GND cap must be 4.7 μF as specified in the datasheet.

4. Could I add a large decoupling capacitor on VIN, as recommended in the datasheet, knowing that I need to meet the USB requirements limiting the capacitor to 1 μF ?

Yes. Usually an OVP IC is added at the front end of the DA9313, this limitation is for the OVP IC.

5. Has the DA9313 got an integrated over-voltage protection (OVP)?

No. The following tiny external OVP devices could be used: [TI TPD1S514](#), [Fairchild FPF2280](#), and [Kinetic KTS1682](#). They all are pinout compatible parts with a very similar feature set.

6. What is the maximum output capacitance allowed at the output of the PVC?

470 μF (it can be distributed).

4.2 Power Voltage Converter

7. What is the allowed maximum DC load current of the PVC?

Typically, it is 8.2A (DC) continuously (10A peak) but it depends on the use case.

DA9313 Frequently Asked Questions

8. What defines the PVC startup time?

The value of the total of the output plus flying capacitors and the startup current set by I_STUP_PVC, configured from 500 mA to 2 A. This assumes no load is drawn during the startup phase.

9. When should I apply a load at the output of the PVC?

Monitor that the PVC output reaches $V_{DD}/2 - 80$ mV before a load greater than half of the I_STUP_PVC value is applied to its output for both standalone and master/slave modes.

In applications where a load is applied during the startup phase, refer to Technical Note ER-PM-003 [2].

10. Could I operate the PVC above 10.5 V?

No. When the PVC is enabled (PVC_EN = 1), V_{IN} must be limited to 10.5 V maximum.

When the PVC is switching, the power MOSFETs are subjected to hot carrier injections and to guarantee the life-time of the product, the maximum drain-to-source voltage is restricted to 10.5 V.

If the PVC is disabled (PVC_EN = 0), 20 V could be applied to V_{IN} assuming that V_{IN} ramp < 1 V/ μ s.

When the PVC is not switching, there is no hot carrier stress. In this case, the maximum drain to source voltage (20 V) is limited by the snap-back characteristics of the power MOSFETs.

11. What is the limitation on the slew rate of the input voltage?

Any voltage applied to V_{IN} has to have a rise time less than < 1 V/ μ s to avoid noise capacitively coupling through the IC.

12. Could I operate the PVC below 5 V?

No. The internal FET drivers operating voltage is 5 V minimum.

4.3 I²C Compatible Interface

13. Could the DA9313 slave be controlled by I²C?

No. The slave I²C lines must be grounded.

14. What is the master/slave interface (MS_IF) protocol on GPIO_0?

GPIO_0, used as MS_IF, voltage domain is V_{CORE}.

- GPIO_0 is asserted high during the PVC ramp up.
- Then it remains low until a load higher than approximately 3 A is applied
- The GPIO_0 then starts toggling to control the switching of the slave's phases; phase 1 and phase 2 in turn. The more load that is applied the more the slave switches between phase 1 and phase 2.
- When the PVC is disabled the master sends a 100 ns shutdown pulse (low) to the slave.
- The slave stops switching, GPIO_0 will then stay high during the duration of the PVC shutdown phase and eventually GPIO_0 will be asserted low.

15. What is the voltage domain of all IOs (GPIOs and I²C) when operating the DA9313 in master/slave?

DA9313 Frequently Asked Questions

All IOs are reference to V_{CORE} (4 V). They may need to be level shifted externally. VDDIO_EN and VDDIO_CONF controls are ignored.

16. What is the master/slave current sharing ratio?

From approximately 3 A both the master and slave start sharing the output load. When the output load reaches approximately 4 A the current sharing is approximately equally distributed.

17. How does the master know when to operate the slave?

By monitoring V_{OUT} and comparing it to the voltage at the master slave interface level (V_{MSI}). This monitoring is used to trigger the slave device via the master/slave interface (MS_IF). The level at which the master triggers the slave is defined in PVC_MS_DROP.

- When the V_{OUT} voltage decreases beyond V_{MSI} due to progressive output loading, the master DA9313 enables the slave DA9313 over MS_IF.
- When the V_{OUT} voltage increases above V_{MSI} + V_{PVC_MS_HYST} (defined in register bits PVC_MS_HYST), the master DA9313 disables the slave DA9313 over MS_IF.

$$V_{MSI} = V_{CCM} - V_{PVC_MS_DROP}$$

Where:

- $V_{CCM} = (V_{BAT}/2 - V_{PVC_DROP} - V_{PVC_HYSTMAX})$
- V_{PVC_HYSTMAX} is a constant value of 30 mV

18. Could I use the master GPIO_1 when operating in master/slave?

Yes. GPIO_1 is used as SLAVE_ID. For the slave, GPIO_1 is connected to its own V_{CORE}. For the master, GPIO_1 must be un-driven by the System on Chip (SoC).

If the master's GPIO_1 is used in open drain (OD) with an external pull-up then Dialog would recommend that the pull-up resistor must be > 820 kΩ to prevent a false SLAVE_ID recognition.

Could I communicate with the DA9313 in POWER_DOWN mode?

No. The host processor should wait for DA9313 to reach the ACTIVE mode following a startup from OFF or POWER_DOWN before starting the I²C communication with DA9313.

19. If I don't use the master or standalone I2C lines, how should I connect them?

If the I²C is not being used, then the I²C lines must be connected to GND.

4.4 Other

20. Could I overdrive the nONKEY pin?

No. The nONKEY port should be never externally overdriven to a voltage higher than V_{CORE} (4 V).

21. Is there a Linux driver available for DA9313?

A Linux driver will be available in March 2017. Please contact ic-support@diasemi.com for technical support.

22. What are the VIH and VIL levels of the integrated GPI Schmitt trigger?

DA9313 Frequently Asked Questions

V_{IH} is 60 % to 67.9 % of IOVDD and V_{IL} is 34.7 % to 40.2 % of IOVDD over PVT (Process Voltage Temperature).

DA9313 Frequently Asked Questions**Revision History**

Revision	Date	Description
2.1	23-Feb-2022	Document rebranded to Renesas.
2.0	30-Oct-2018	Additional descriptions.
Change details: <ul style="list-style-type: none">● Section 4.2: Power Voltage Converter<ul style="list-style-type: none">○ Additional information to questions 8, 9, and 10○ New question (11) and answer		
1.0	21-Feb-2017	Initial version.

DA9313 Frequently Asked Questions

Status Definitions

Status	Definition
DRAFT	The content of this document is under review and subject to formal approval, which may result in modifications or additions.
APPROVED or unmarked	The content of this document has been approved for publication.

DA9313 Frequently Asked Questions

Important Notice and Disclaimer

RENESAS ELECTRONICS CORPORATION AND ITS SUBSIDIARIES ("RENESAS") PROVIDES TECHNICAL SPECIFICATIONS AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS OR IMPLIED, INCLUDING, WITHOUT LIMITATION, ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for developers skilled in the art designing with Renesas products. You are solely responsible for (1) selecting the appropriate products for your application, (2) designing, validating, and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. Renesas grants you permission to use these resources only for development of an application that uses Renesas products. Other reproduction or use of these resources is strictly prohibited. No license is granted to any other Renesas intellectual property or to any third party intellectual property. Renesas disclaims responsibility for, and you will fully indemnify Renesas and its representatives against, any claims, damages, costs, losses, or liabilities arising out of your use of these resources. Renesas' products are provided only subject to Renesas' Terms and Conditions of Sale or other applicable terms agreed to in writing. No use of any Renesas resources expands or otherwise alters any applicable warranties or warranty disclaimers for these products.

© 2022 Renesas Electronics Corporation. All rights reserved.

(Rev.1.0 Mar 2020)

Corporate Headquarters

TOYOSU FORESIA, 3-2-24 Toyosu

Koto-ku, Tokyo 135-0061, Japan

www.renesas.com

Contact Information

For further information on a product, technology, the most up-to-date version of a document, or your nearest sales office, please visit:

<https://www.renesas.com/contact/>

Trademarks

Renesas and the Renesas logo are trademarks of Renesas Electronics Corporation. All trademarks and registered trademarks are the property of their respective owners.

IMPORTANT NOTICE AND DISCLAIMER

RENESAS ELECTRONICS CORPORATION AND ITS SUBSIDIARIES (“RENESAS”) PROVIDES TECHNICAL SPECIFICATIONS AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES “AS IS” AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS OR IMPLIED, INCLUDING, WITHOUT LIMITATION, ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, OR NON-INFRINGEMENT OF THIRD-PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for developers who are designing with Renesas products. You are solely responsible for (1) selecting the appropriate products for your application, (2) designing, validating, and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. Renesas grants you permission to use these resources only to develop an application that uses Renesas products. Other reproduction or use of these resources is strictly prohibited. No license is granted to any other Renesas intellectual property or to any third-party intellectual property. Renesas disclaims responsibility for, and you will fully indemnify Renesas and its representatives against, any claims, damages, costs, losses, or liabilities arising from your use of these resources. Renesas' products are provided only subject to Renesas' Terms and Conditions of Sale or other applicable terms agreed to in writing. No use of any Renesas resources expands or otherwise alters any applicable warranties or warranty disclaimers for these products.

(Disclaimer Rev.1.01 Jan 2024)

Corporate Headquarters

TOYOSU FORESIA, 3-2-24 Toyosu,
Koto-ku, Tokyo 135-0061, Japan
www.renesas.com

Trademarks

Renesas and the Renesas logo are trademarks of Renesas Electronics Corporation. All trademarks and registered trademarks are the property of their respective owners.

Contact Information

For further information on a product, technology, the most up-to-date version of a document, or your nearest sales office, please visit www.renesas.com/contact-us/.